



Technician License Course



Technician License Course

Chapter 3

Lesson Plan Module - 6

Electrical Components


Electronics – Controlling the Flow of Current

- To make an electronic device (like a radio) do something useful (like a receiver), we need to control and manipulate the flow of current.
- There are a number of different electronic components that are used to do this

Schematic Diagrams

- We can draw pictures of electronic components forming circuits, such as for the parallel and series circuit examples. This is too cumbersome for most circuits.
- Schematic diagrams use symbols with different components, each having a different symbol.




Schematic Diagrams

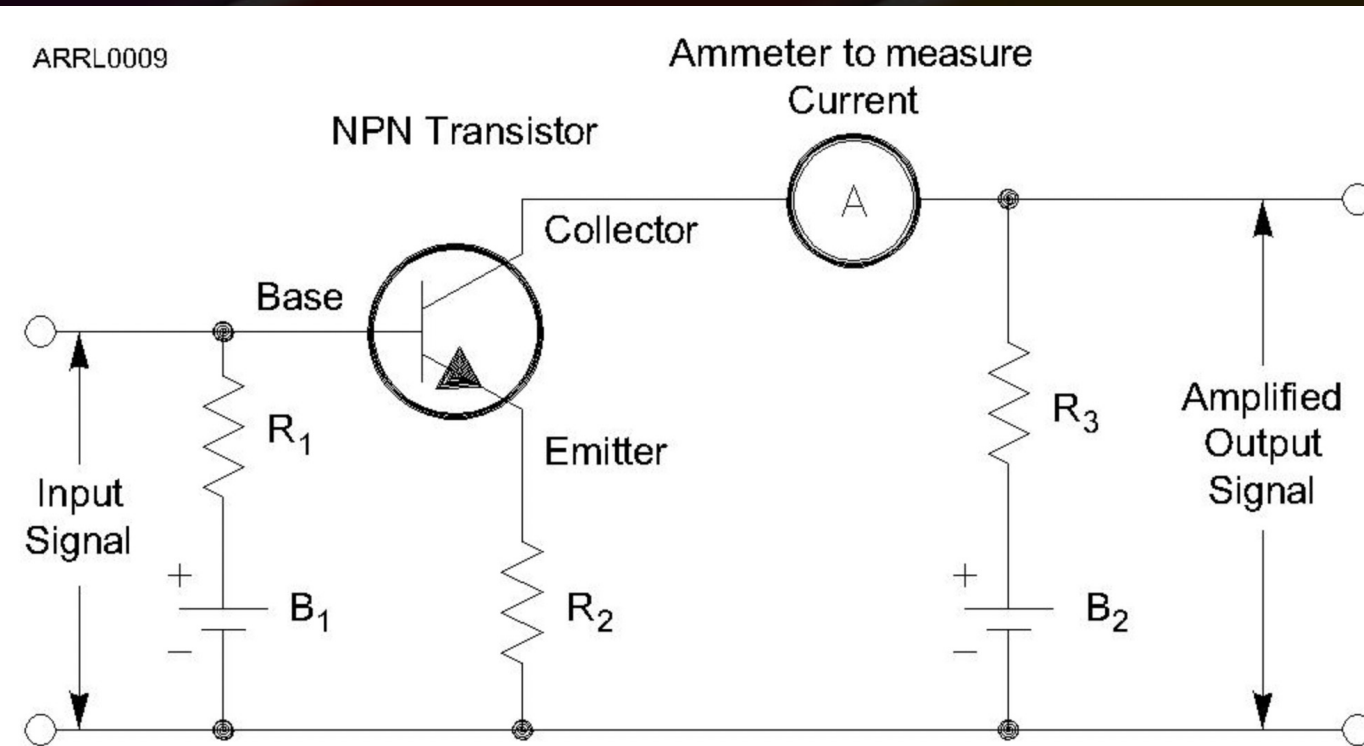

The lines and dots on schematics represent electrical connections between the components.

The Resistor

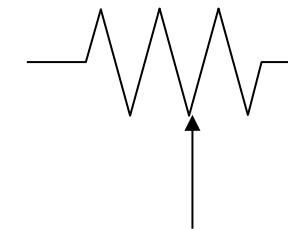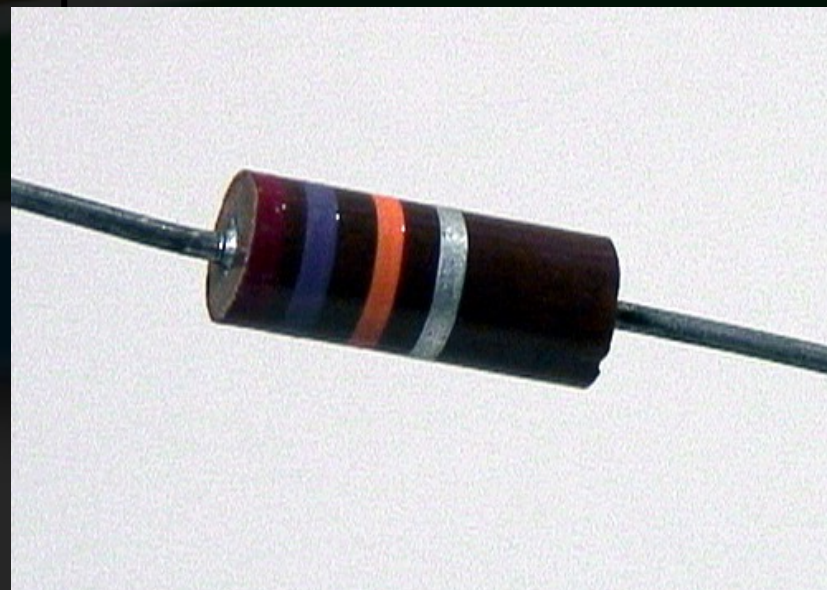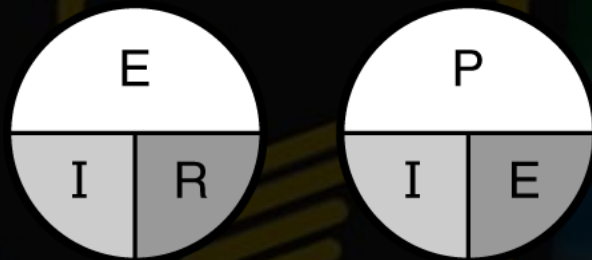- The function of a resistor is to restrict the flow of current.
- Remember Ohm's Law:
- Schematic symbol





Potentiometer
or "Pot"

Arrow indicates adjustable value,
such as for a volume control.

The Capacitor

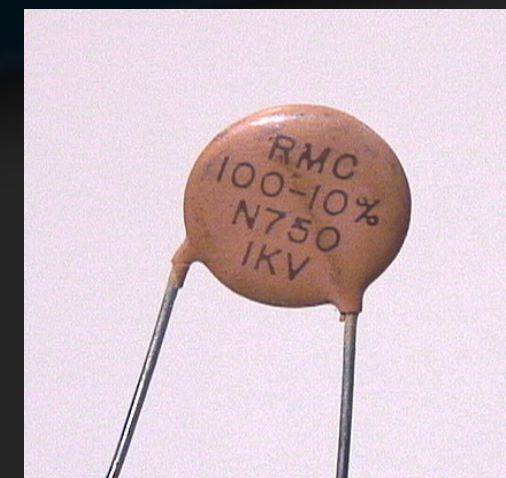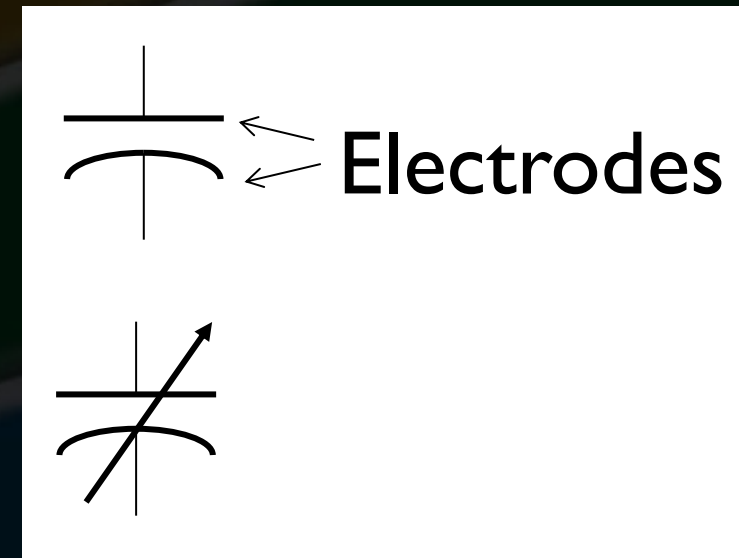- The function of a capacitor is to store electrical energy – called *capacitance*.
 - Acts like a battery
 - Stores energy in an electric field created by voltage between the electrodes with insulating *dielectric* material between them
- Schematic symbol



The Inductor


- The function of an inductor is to store magnetic energy – called *inductance*.
 - A coil of wire around a *core* of air or magnetic material like iron or ferrite
 - Stores energy in a magnetic field created by current in the wire
- Schematic symbol



The Transformer

- A pair of inductors sharing a common core
 - Also share their magnetic field
 - Used to transfer energy from one circuit to another without a direct connection
 - Changes the ratio of voltage and current

- Schematic symbol

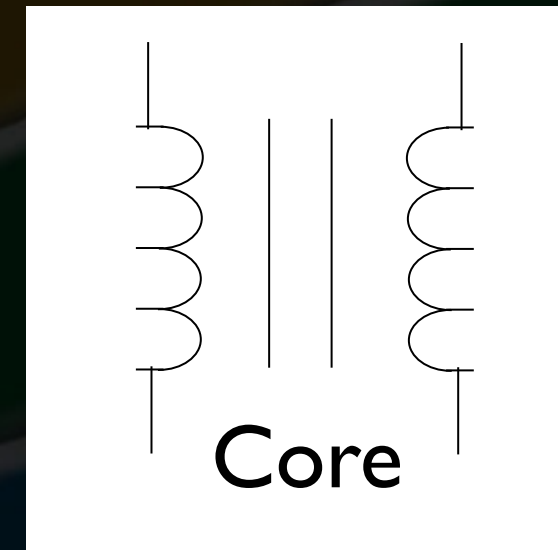


Electrical Units

- Each type of component has a value measured in specific units:
 - Resistors > resistance > ohms (Ω)
 - Capacitors > capacitance > farads (F)
 - Inductors > inductance > henrys (H)

Component Designators

- Each schematic symbol has a *designator* to denote which component it refers to. For example, the 10th resistor in a circuit is R10.
- Resistors (R), capacitors (C), inductors (L).

Component Designators

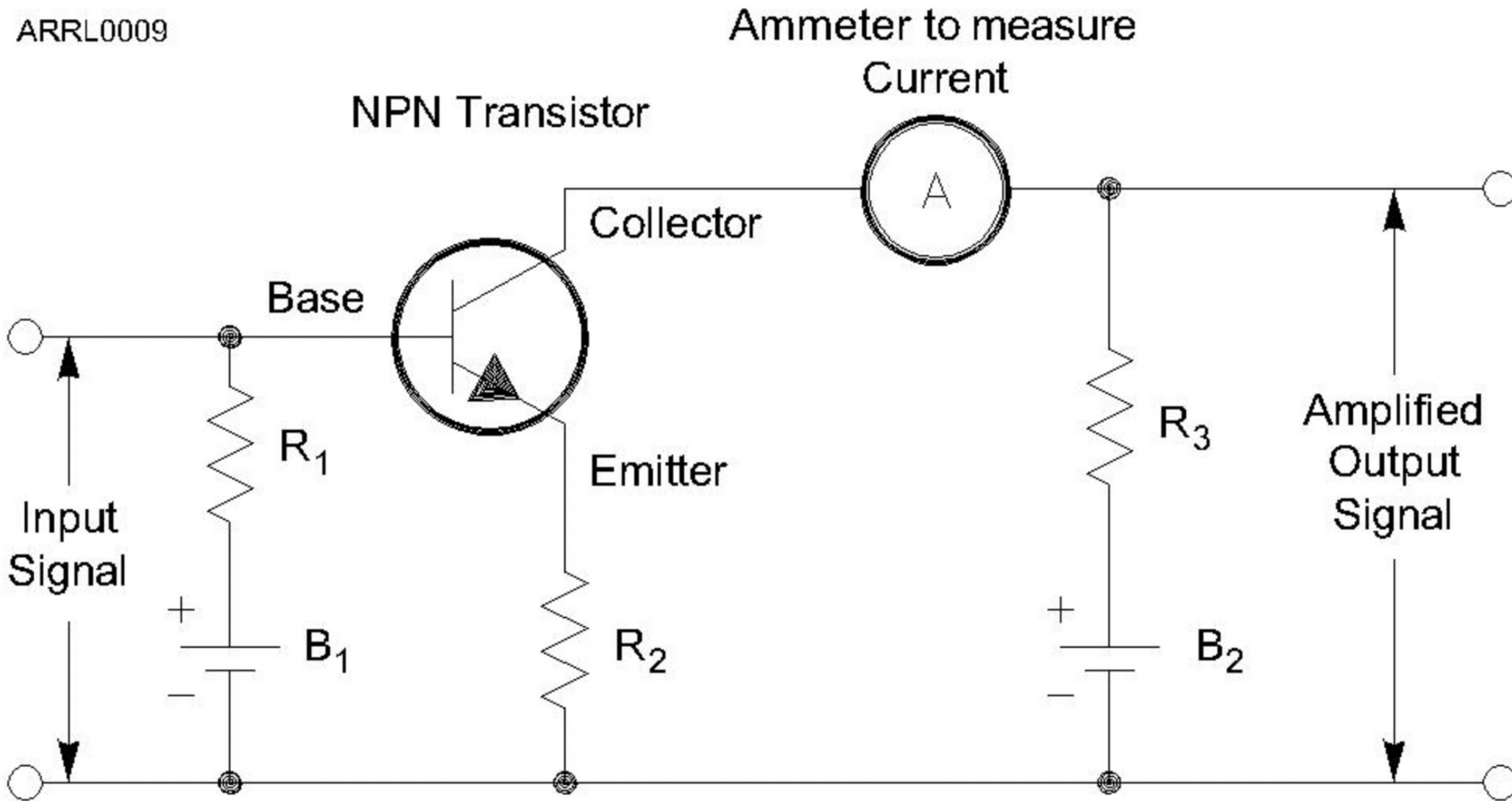

Indicators and Displays

- Indicators communicate status
 - ON/OFF, ready/stand-by, left/right
 - LEDs, light bulbs, symbols, audio tones
- Displays communicate values or text
 - Numeric values, warnings, messages
 - Digital and analog meters, LCD screens

Reactance

- Capacitors and inductors store energy, rather than dissipating it like resistors.
- Energy storage creates an effect called *reactance* (symbol X) that acts like a resistance in opposing the flow of ac current.
 - Capacitors create *capacitive reactance* (X_C)
 - Inductors create *inductive reactance* (X_L)
 - The effects of each are complementary

Impedance


- The combination of resistance (R) and reactance (X) is called *impedance*, represented by the symbol Z .
- Impedance represents a circuit's opposition to both ac and dc currents.

Resonance

- A component's reactance depends on frequency: X_L increases with frequency while X_C decreases.
- At the frequency for which a circuit's X_L and X_C are equal, their effects cancel. This is the circuit's *resonant frequency*.
- At *resonance*, a circuit has only resistance, which affects ac and dc current equally.

Resonant or Tuned Circuit

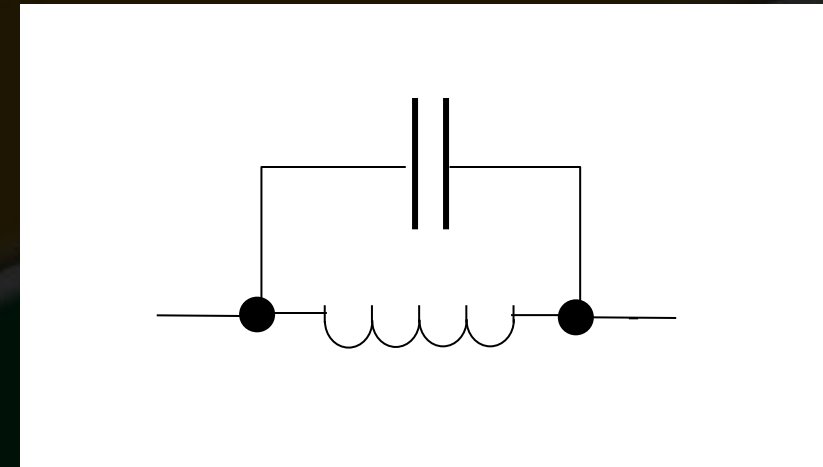- Capacitors and inductors connected together create a *tuned circuit*.
- When X_L and X_C are equal, the circuit is *resonant*.
- If C or L are adjustable the resonant frequency can be varied or tuned.




Semiconductor Components

- Made of material like silicon that are “OK” conductors but not as good as metals.
- Impurities added to semiconductors create material with more than usual electrons (*N-type*) and fewer than usual (*P-type*) electrons.
- Structures of N and P material can control current flow through the semiconductor.


The Diode

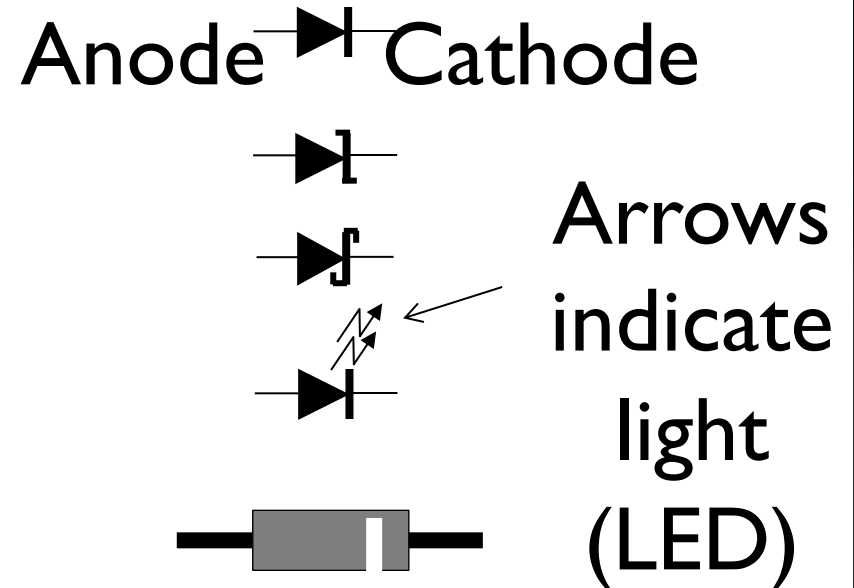- Allows current to flow in only one direction.
 - Two electrodes: *anode* and *cathode*
 - AC current is changed to varying pulses of dc – called *rectification*
 - Diodes used to change ac power to dc power are called *rectifiers*
- Schematic symbol
- Designator (D or CR)




The Transistor

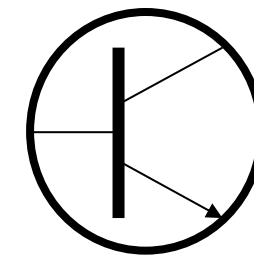- The function of a transistor is to control large signals with small ones.
 - An “electronically controlled current valve”
 - When used as an amplifier a transistor produces *gain*
 - Transistors can also be used as a switch
- Schematic symbol
 - Designator (Q)




Bipolar Junction Transistor (BJT)

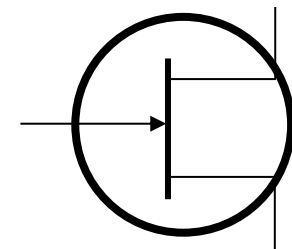

Field-Effect Transistor (FET)

The Transistor

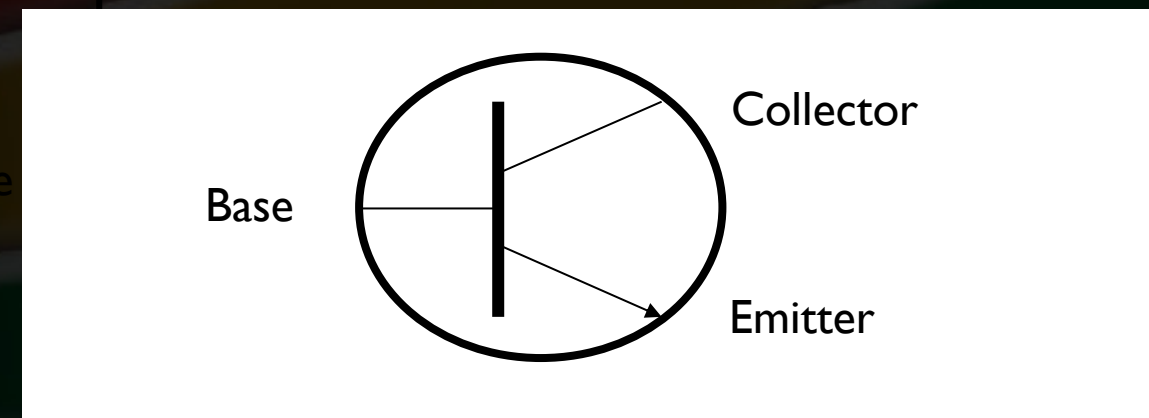
- The Bipolar Junction Transistor (BJT) has three layers of N or P material connected to electrodes:



- Depending on the arrangement of layers, a BJT is either an NPN or PNP transistor.

The Transistor



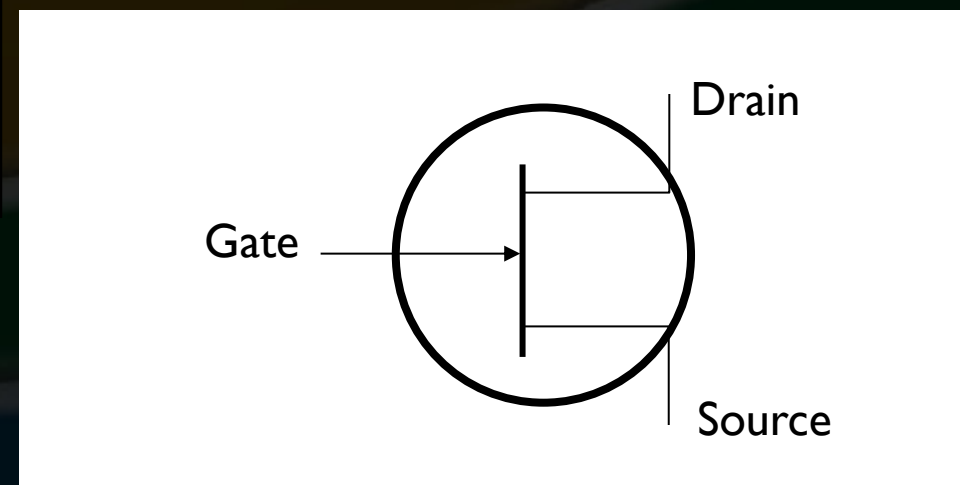
- The Field-Effect Transistor (FET) has a conducting path or channel of N and P material connected to the drain and source electrodes.



- Voltage applied to the gate electrode controls current through the channel.

The Integrated Circuit

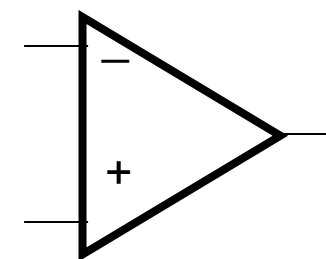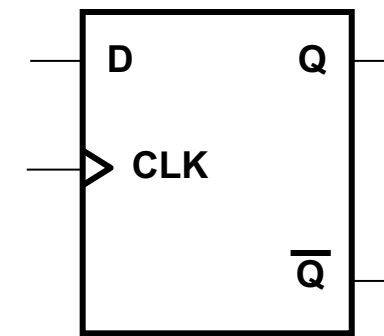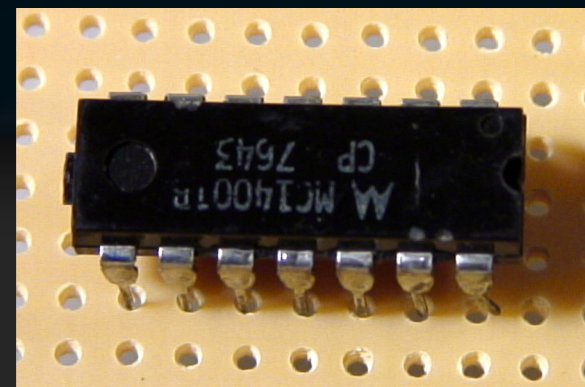- The integrated circuit is a collection of components contained in one device that accomplishes a specific task.
- Schematic symbol
- Designator (IC or U)



Protective Components

- Fuses and circuit breakers are designed to remove power in case of a circuit overload.
 - Fuses blow – one time protection
 - Circuit breakers trip – can be reset and reused
 - Always use proper rating
- Schematic symbol
- Designator (F or CB)



Fuses




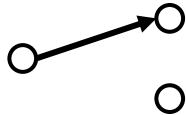
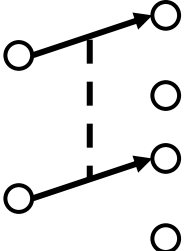
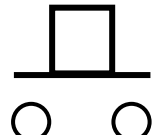
Circuit
Breaker



Switches


- Switches are used to interrupt or allow current to flow.
- Each circuit controlled by the switch is a *pole*
- Each position is called a *throw*

- Schematic symbol
- Designator (S or SW)

	SPST
	SPDT
	DPDT
	Pushbutton

Relays


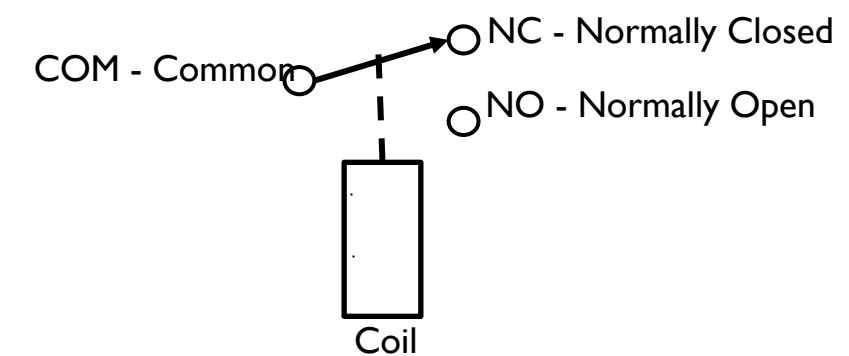
- Relays are switches activated by current in a coil (electromagnet)
 - Relays use the same pole/throw names as switches
 - The moving switch is called the *armature*
 - *Contacts* are named by when they are connected
- Schematic symbol
 - Designator (K or RLY)



Other Circuit Symbols

Schematic Symbols Used in Circuit Diagrams

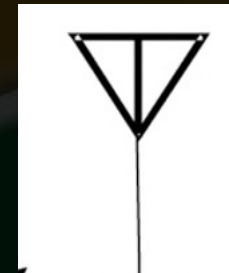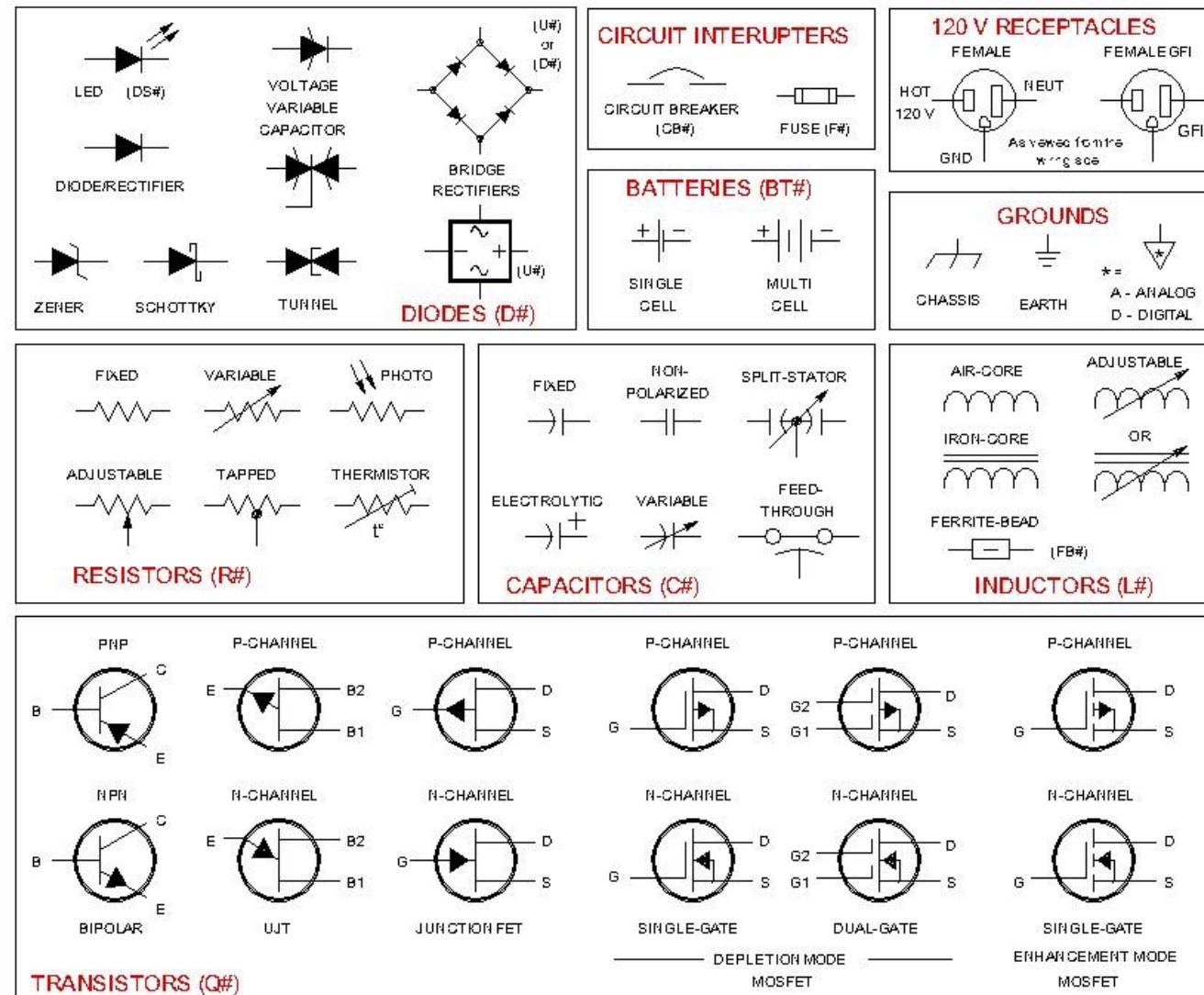Labelling conventions: # is a sequential number. (X#) is the component designator. Examples - C3, L11, R8, Q3



Antenna



Practice Questions

What is the ability to store energy in an electric field called?

Base



What is the ability to store energy in an **electric field** called?

Capacitance

Base



What is the basic unit of capacitance?

Base



What is the basic unit of capacitance?

The farad

Base



What is the ability to store energy in a magnetic field called?

Base



What is the ability to store energy in a **magnetic field** called?

Inductance

Base



What is the basic unit of inductance?

Base



What is the basic unit of inductance?

The henry

Base



What is meant by the term impedance?

Base

The image shows a cross-section of a multi-layer printed circuit board (PCB) with various colored layers. On the left, a yellow triangular callout box contains circuit symbols for an inductor (L), a capacitor (C), and a resistor (R). An arrow labeled 'Base' points to the bottom layer of the PCB stack-up.

What is meant by the term impedance?

It is a measure of the opposition to AC current flow in a circuit

base



What are the units of impedance?

Base



What are the units of impedance?

Ohms

Base



What electrical component is used to oppose the flow of current in a DC circuit?

Base



What electrical component is used to oppose the flow of current in a DC circuit?

Resistor

Base



What type of component is often used as an adjustable volume control?

Base



What type of component is often used as an adjustable volume control?

Potentiometer

Base



What electrical parameter is controlled by a potentiometer?

Base



What electrical parameter is controlled by a potentiometer?

Resistance

Base



What electrical component stores energy in an electric field?

Base



What electrical component stores energy in an electric field?

Capacitor

Base



What type of electrical component consists of two or more conductive surfaces separated by an insulator?


Base



What type of electrical component consists of two or more conductive surfaces separated by an insulator?

Capacitor

Base

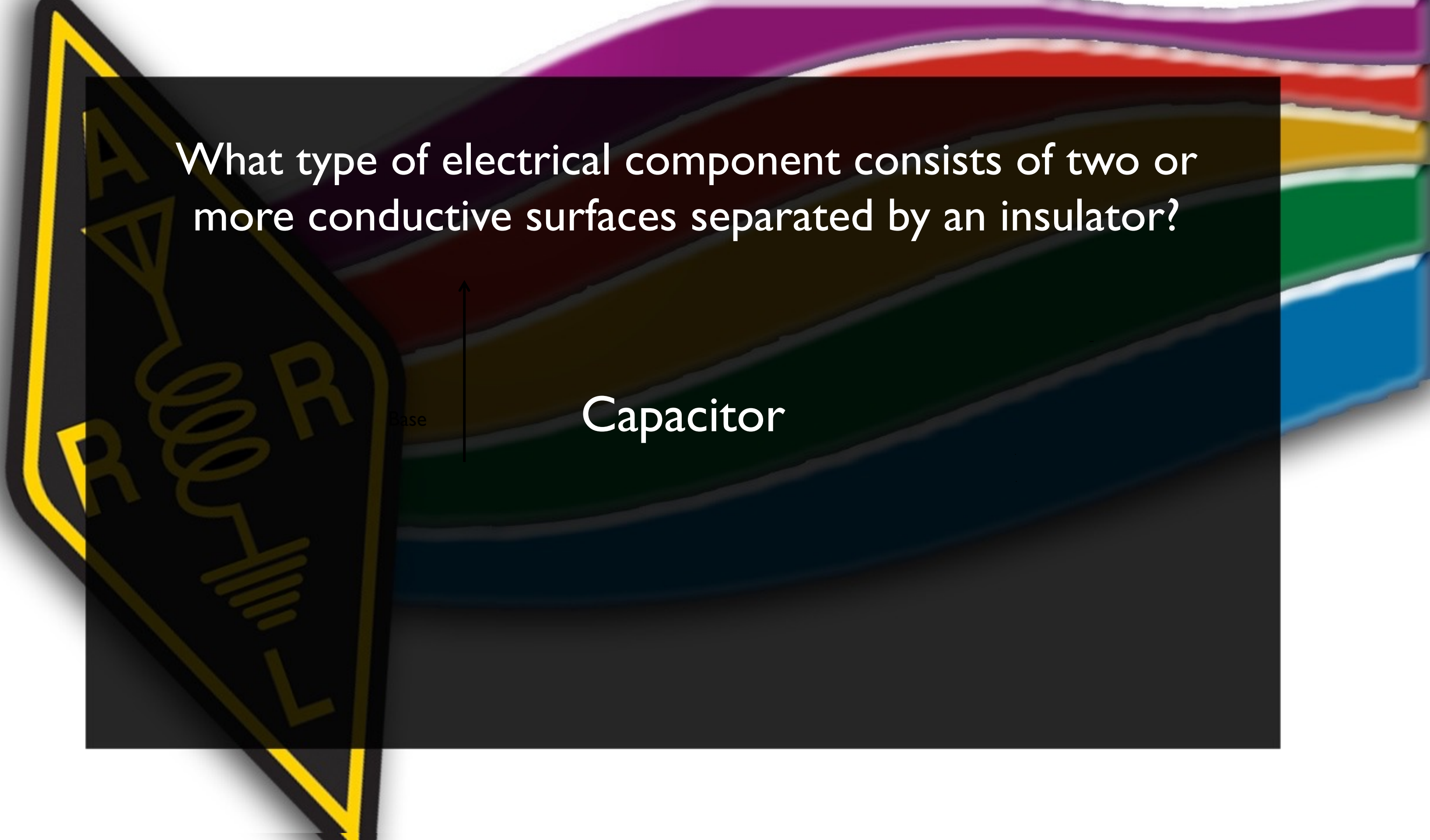

What type of electrical component stores energy in a magnetic field?

Base



What type of electrical component stores energy in a magnetic field?

Inductor

Base



What electrical component is usually composed of a coil of wire?

Base



What electrical component is usually composed of a coil of wire?

Inductor

Base



What electrical component is used to connect or disconnect electrical circuits?

Base

A vertical arrow points upwards from the word 'Base' to the middle region of a transistor symbol, which is partially visible on the left side of the image. The transistor symbol is a triangle with a circle inside, and the word 'Base' is written next to it.

What electrical component is used to connect or disconnect electrical circuits?


Switch

Base



What electrical component is used to protect other circuit components from current overloads?


Base

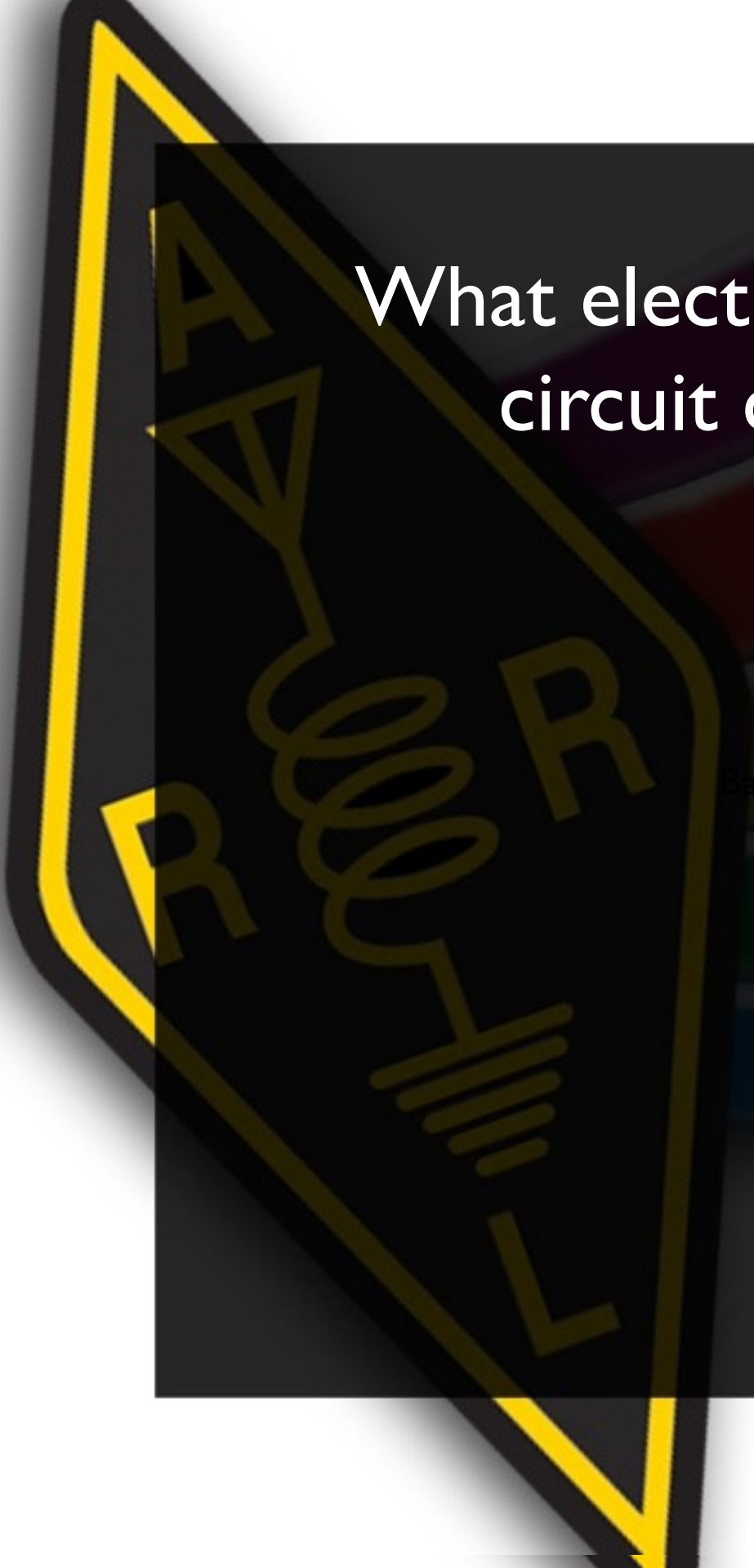

What electrical component is used to protect other circuit components from current overloads?


Fuse

Base

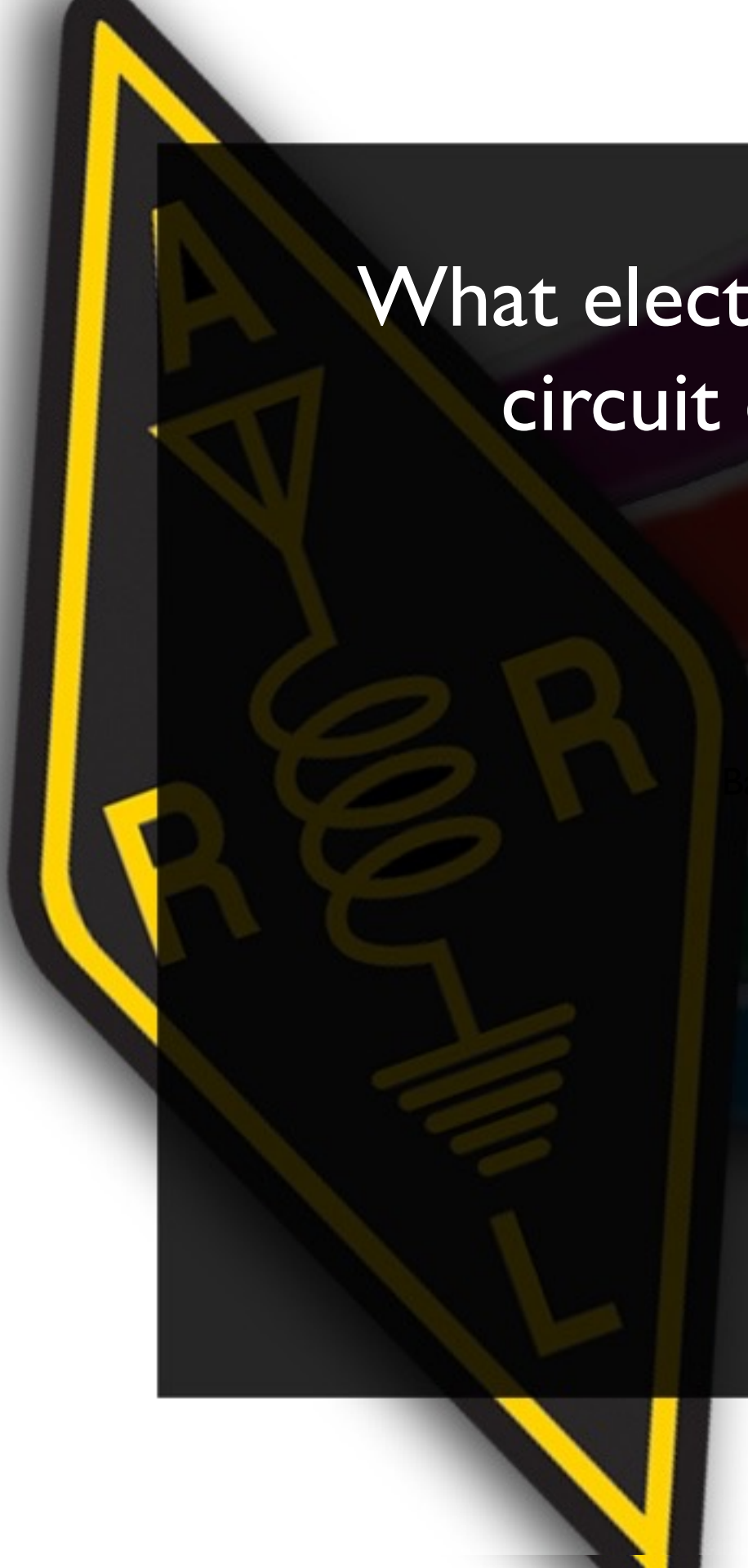

What class of electronic components is capable of using a voltage or current signal to control current flow?

Base

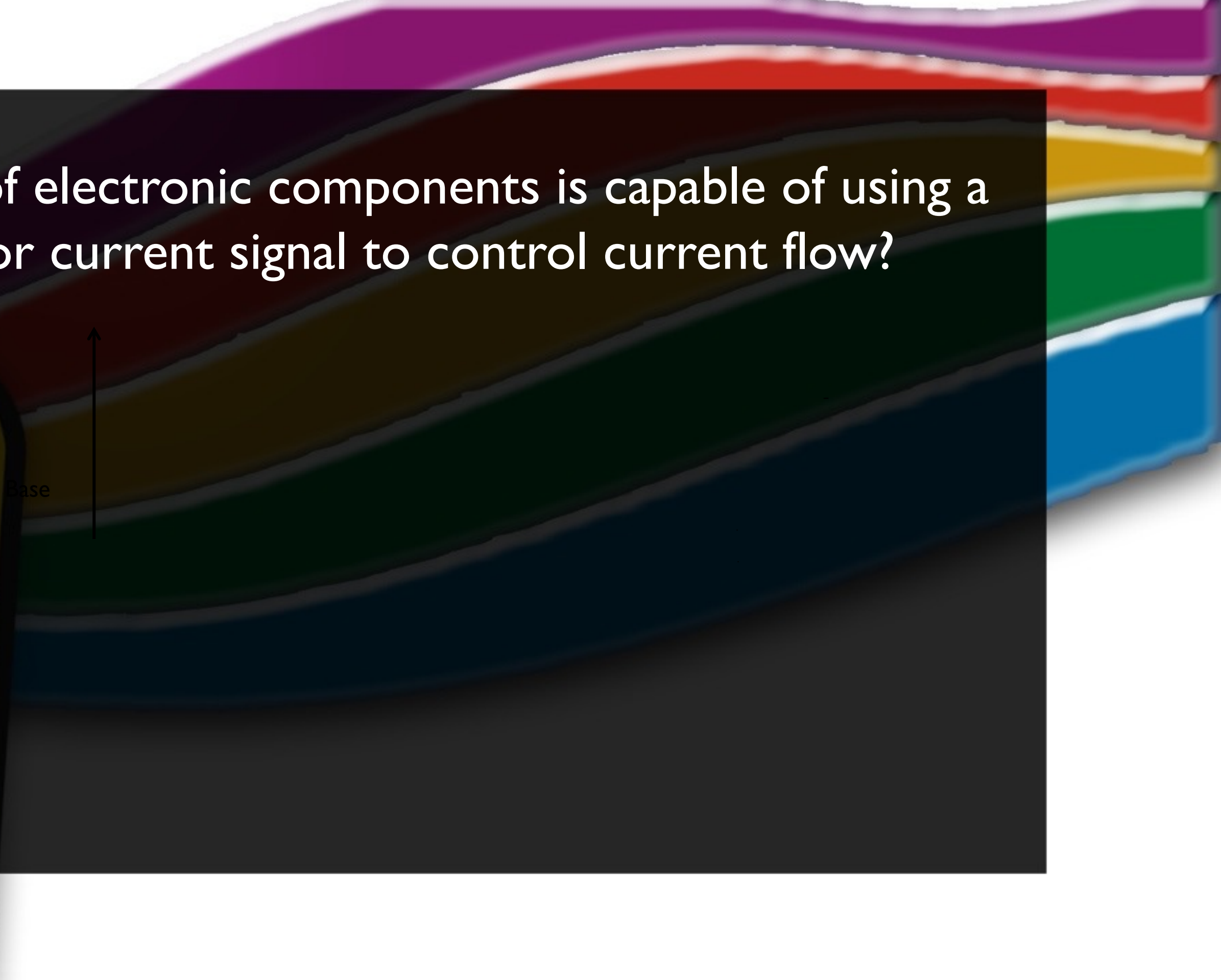

What class of electronic components is capable of using a voltage or current signal to control current flow?


Transistors

Base



What electronic component allows current to flow in only one direction?

Base

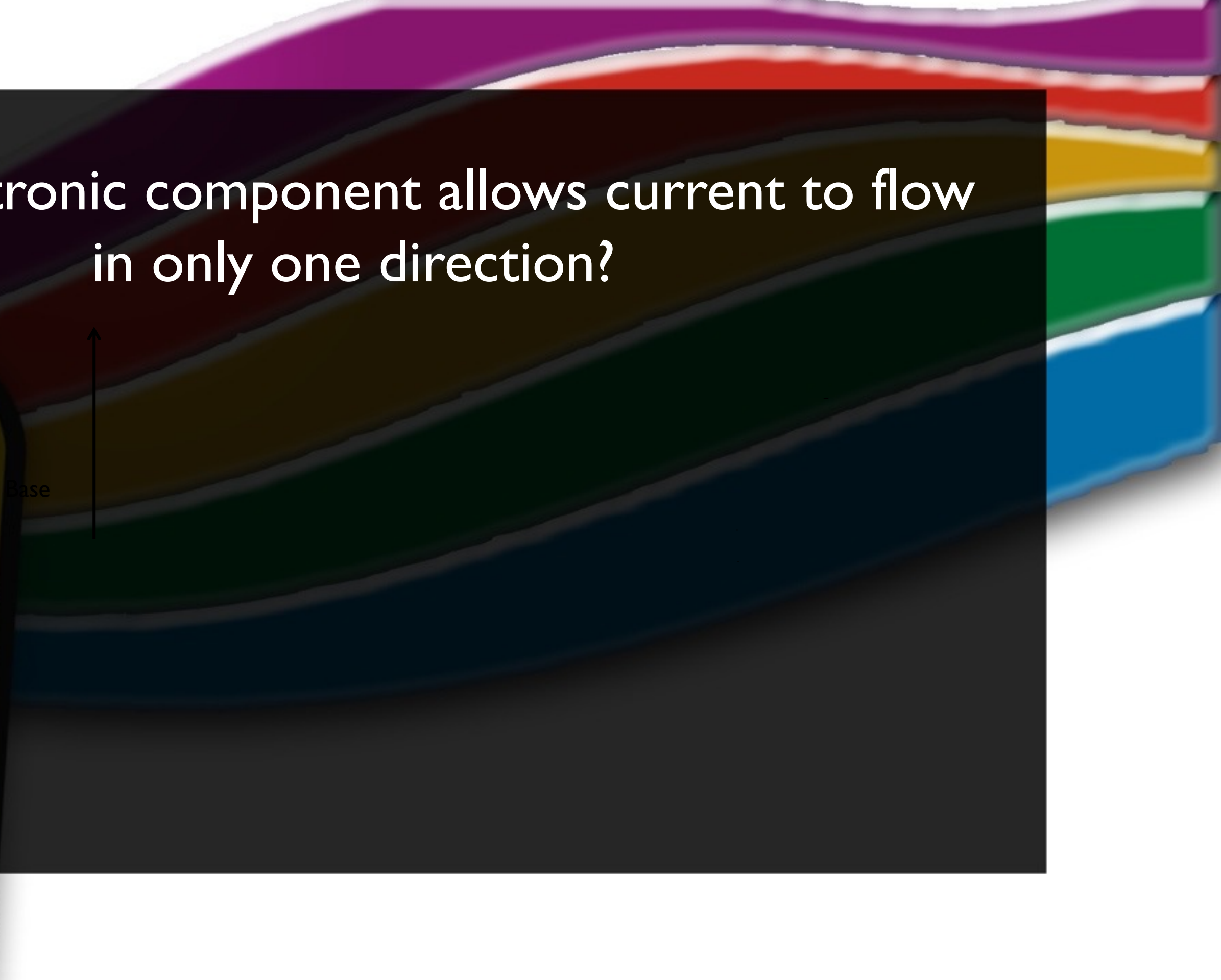

What electronic component allows current to flow in only one direction?

Diode

Base



Which of these components can be used as an electronic switch or amplifier?

Base



Which of these components can be used as an electronic switch or amplifier?

Transistor

Base



Which of the following components can be made of three layers of semiconductor material?

Base



Which of the following components can be made of three layers of semiconductor material?

Transistor

Base



Which of the following electronic components can amplify signals?

Base



Which of the following electronic components
can amplify signals?

Transistor

Base



How is the cathode lead of a semiconductor diode usually identified?

Base

A diagram of a semiconductor diode is shown. The diode has a cylindrical body with a rainbow-colored band on one end, which is the cathode lead. An arrow points from the word 'Base' to the band.

How is the cathode lead of a semiconductor diode usually identified?

With a stripe

Base



What does the abbreviation LED stand for?


Base



What does the abbreviation LED stand for?

Light Emitting Diode

Base

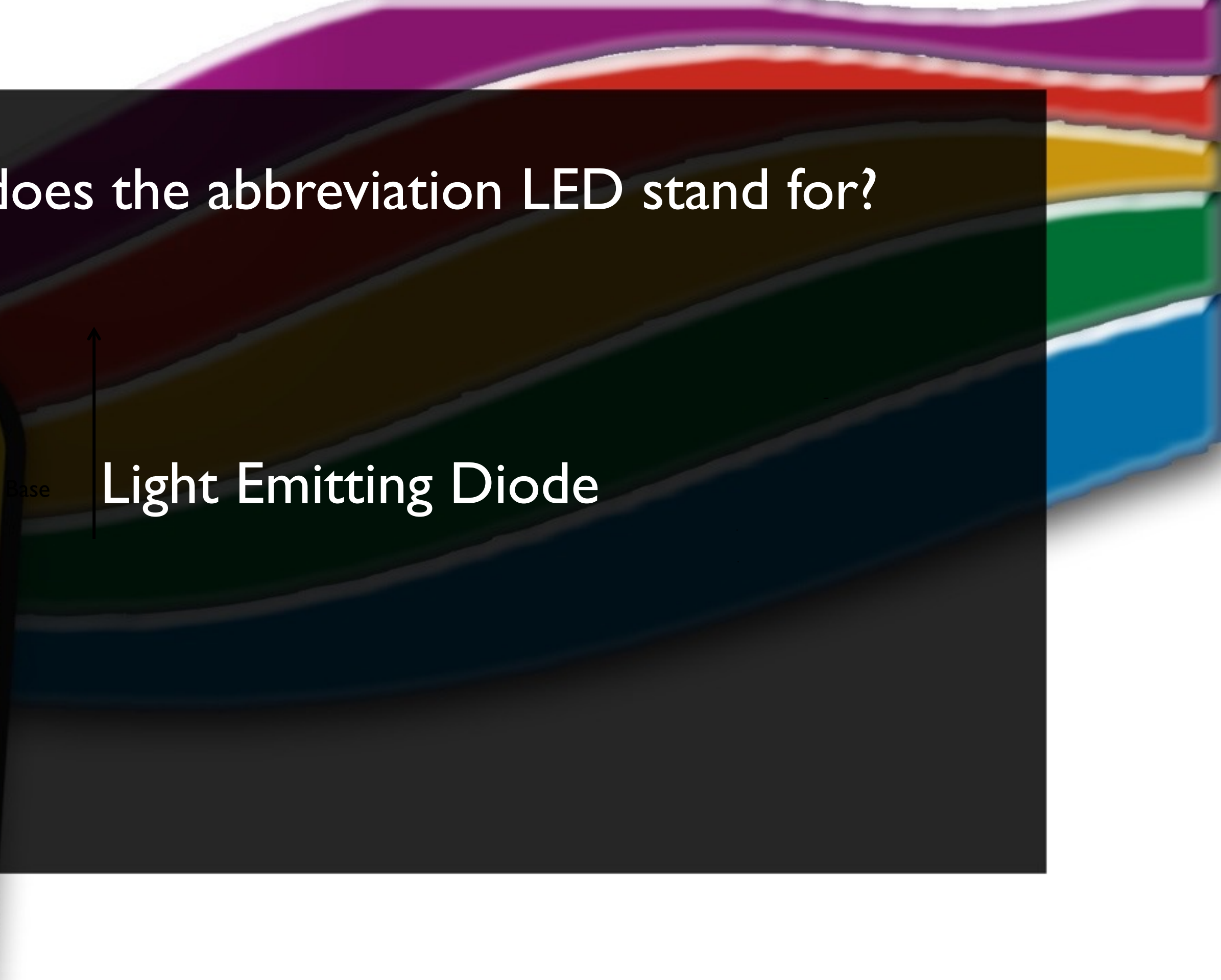

What does the abbreviation FET stand for?

Base



What does the abbreviation FET stand for?

Field Effect Transistor

Base



What are the names of the two electrodes of a diode?

Base



What are the names of the two electrodes of a diode?

Anode and cathode

Base



What are the three electrodes of a PNP or NPN transistor?

Base



What are the three electrodes of a PNP or NPN transistor?

Emitter, base, and collector



What are the three electrodes of a field effect transistor?

Base



What are the three electrodes of a field effect transistor?

Source, gate, and drain

Base



What is the term that describes a transistor's ability to amplify a signal?

Base



What is the term that describes a transistor's ability to amplify a signal?

Gain

Base



What is the name for standardized representations of components in an electrical wiring diagram?

Base



What is the name for standardized representations of components in an electrical wiring diagram?

Schematic symbols

Base



What is component 1 in figure T1?

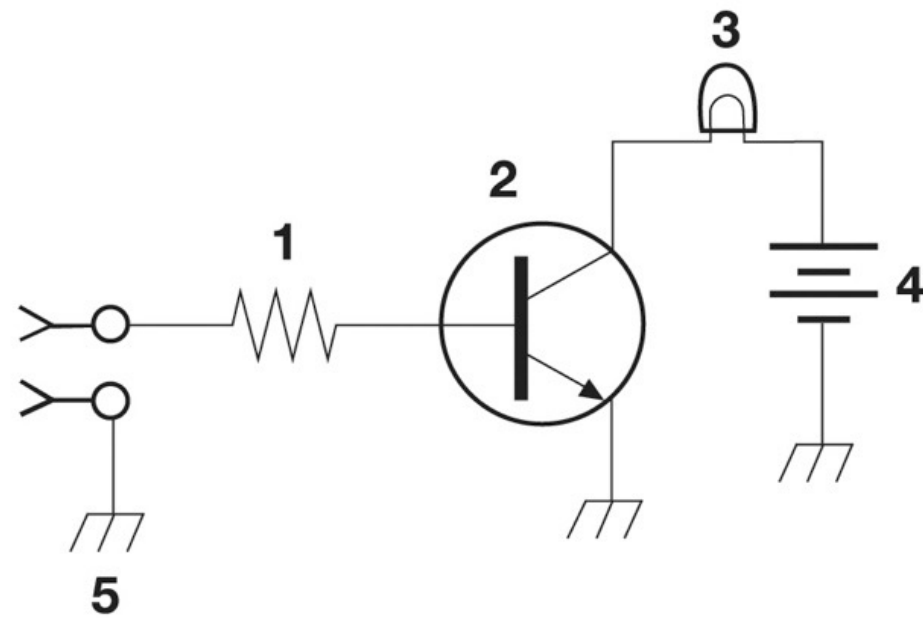


Figure T-1

What is component 1 in figure T1?

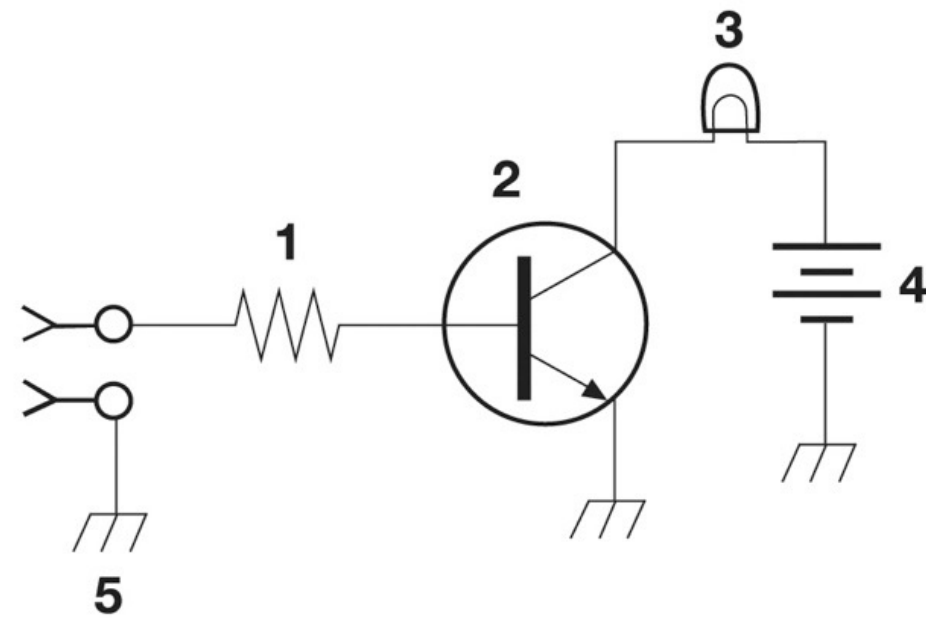


Figure T-1

Resistor

What is component 2 in figure T1?

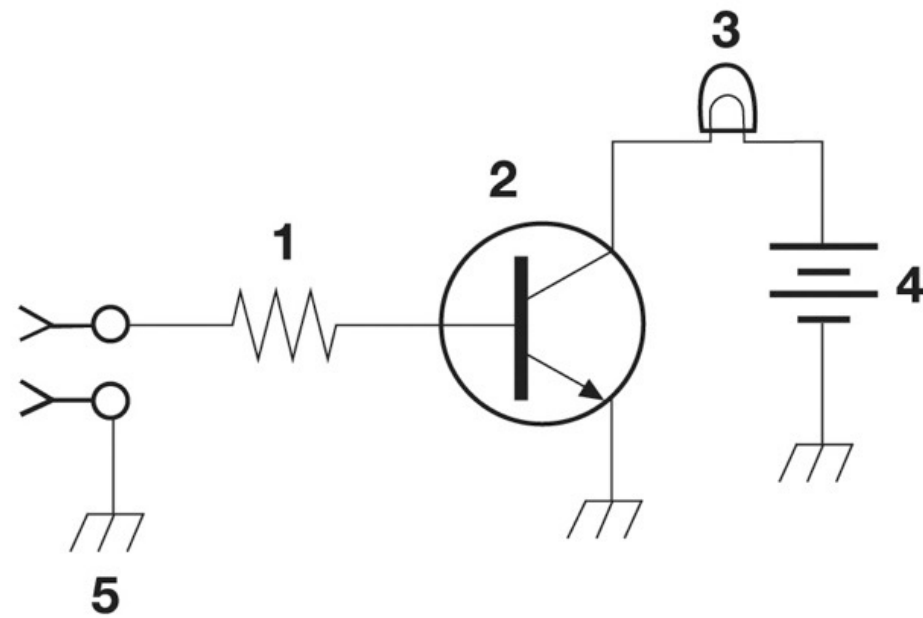


Figure T-1

What is component 2 in figure T1?

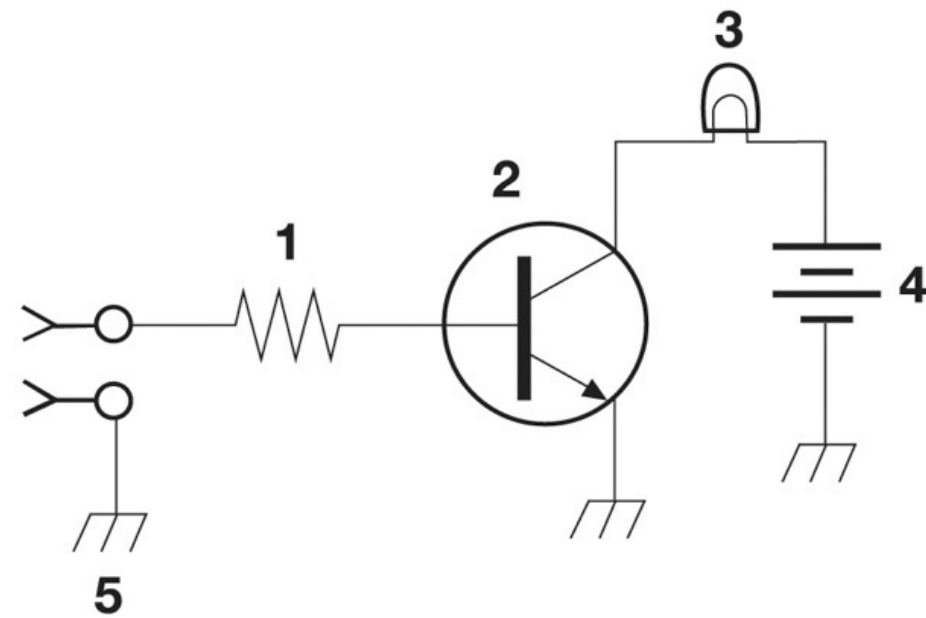


Figure T-1

Transistor

What is component 3 in figure T1?

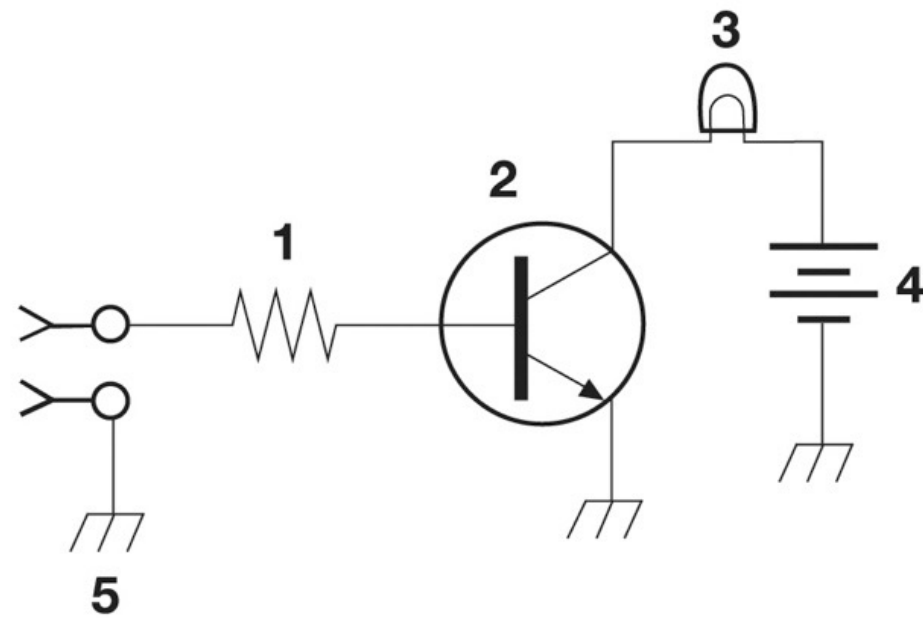


Figure T-1

What is component 3 in figure T1?

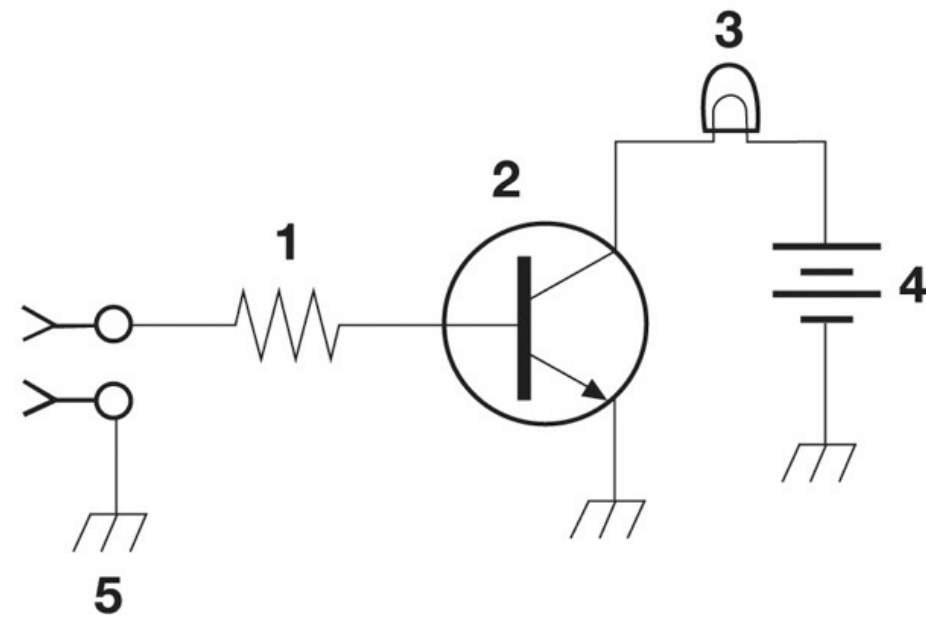


Figure T-1

Lamp

What is component 4 in figure T1?

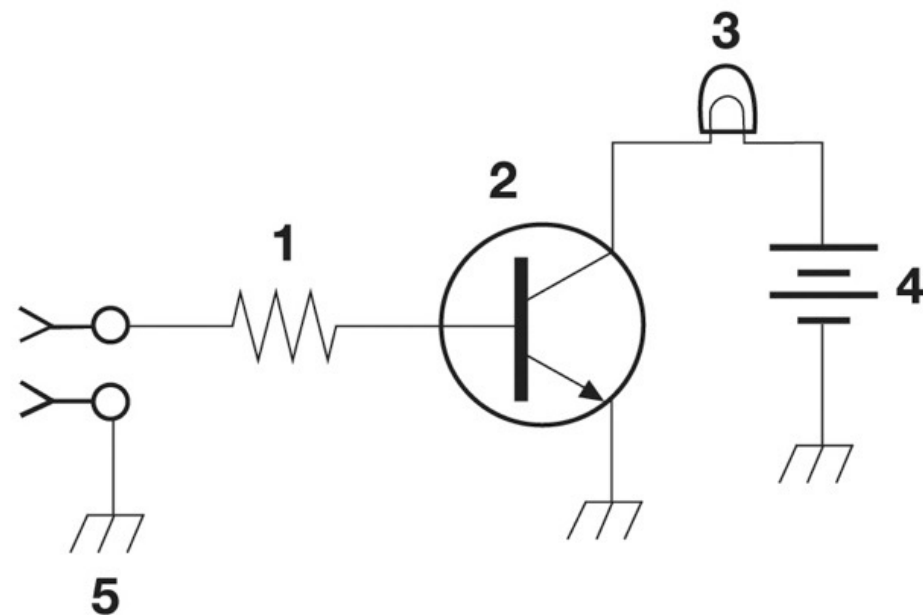


Figure T-1

What is component 4 in figure T1?

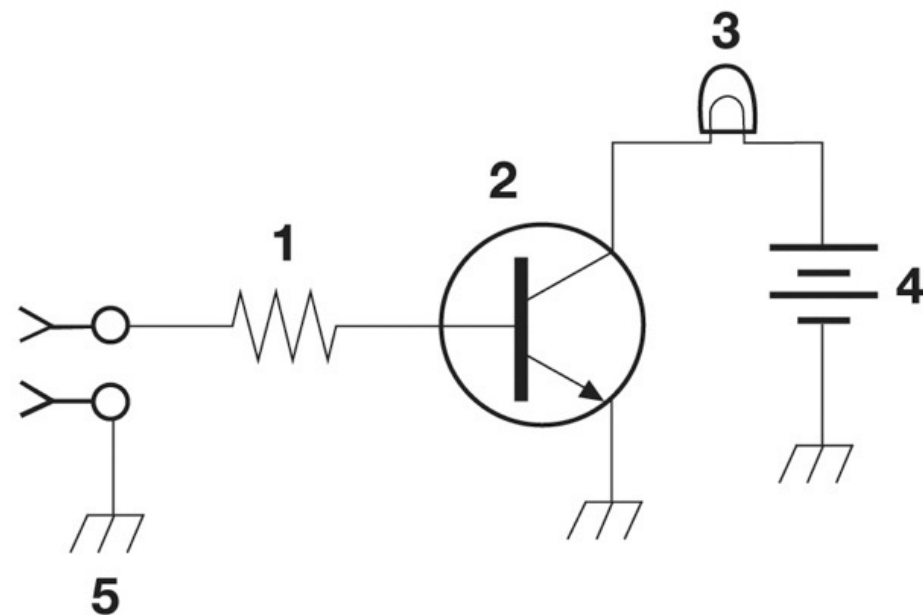


Figure T-1

Battery

What is component 6 in figure T2?

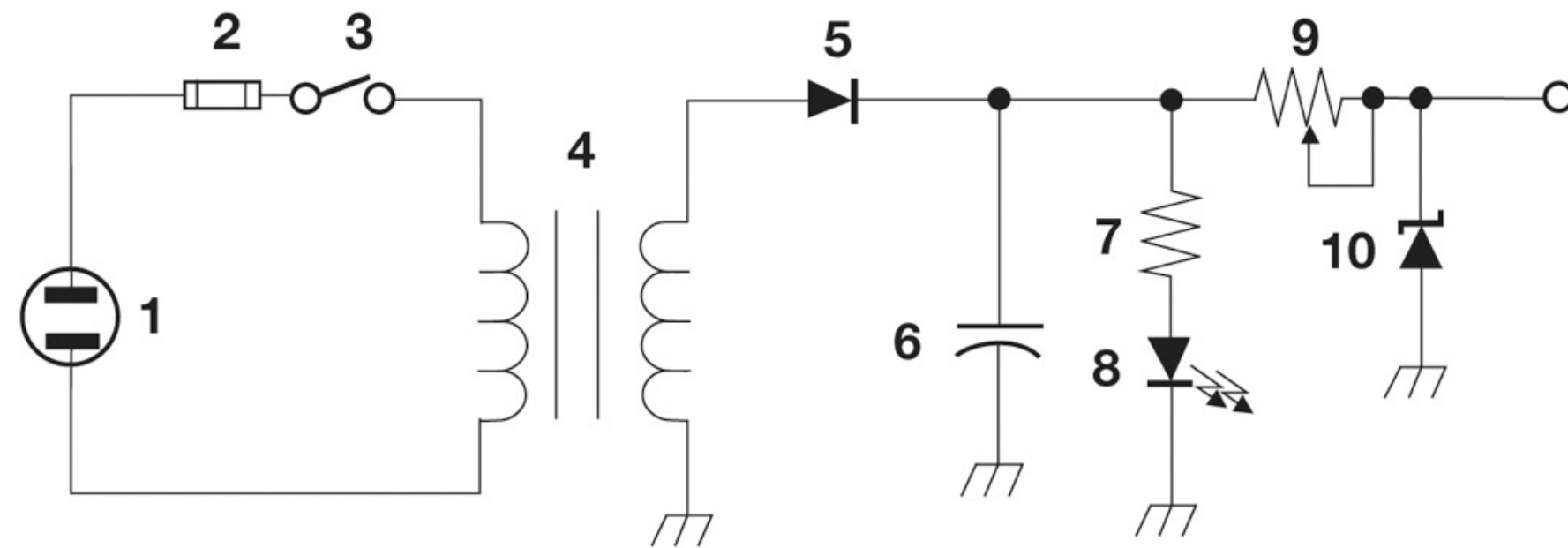


Figure T-2

What is component 6 in figure T2?

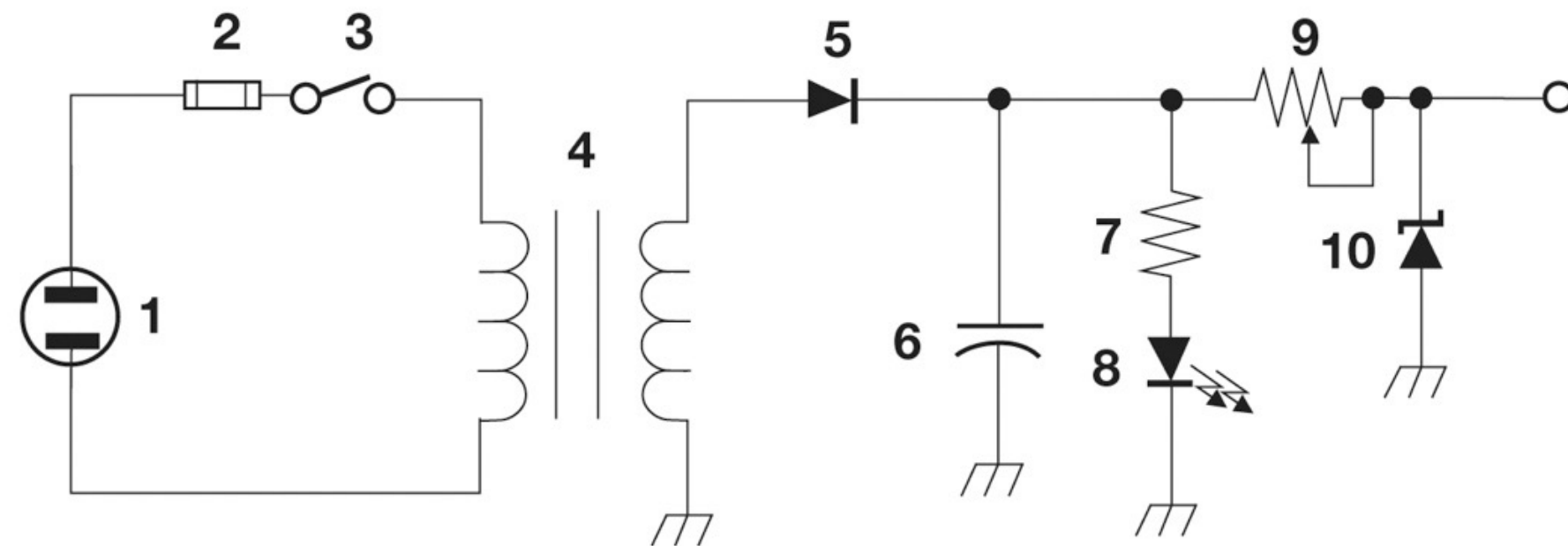


Figure T-2

Capacitor

What is component 8 in figure T2?

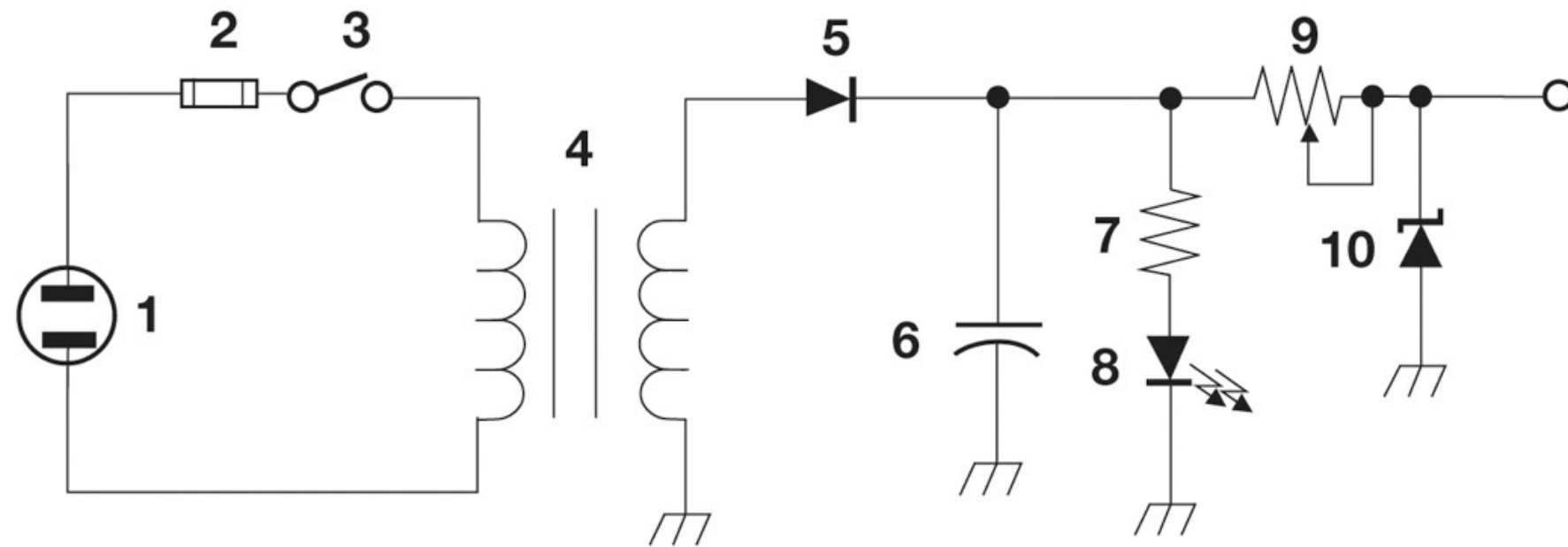


Figure T-2

What is component 8 in figure T2?

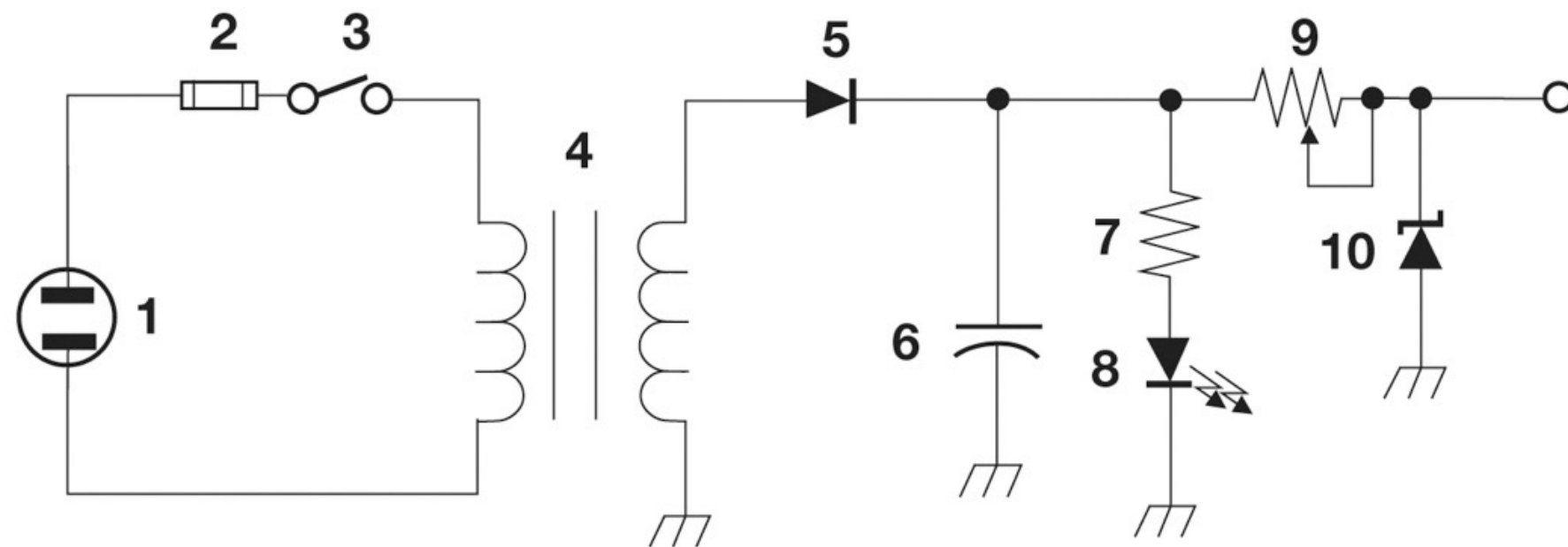


Figure T-2

Light emitting diode

What is component 9 in figure T2?

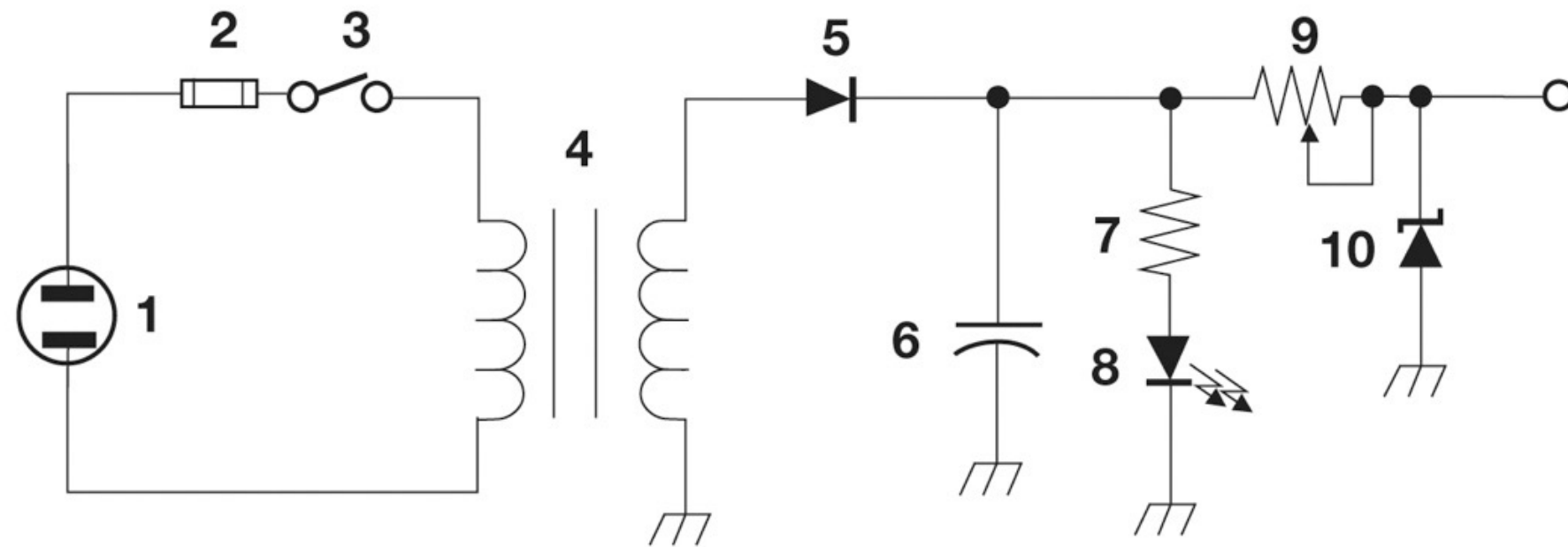


Figure T-2

What is component 9 in figure T2?

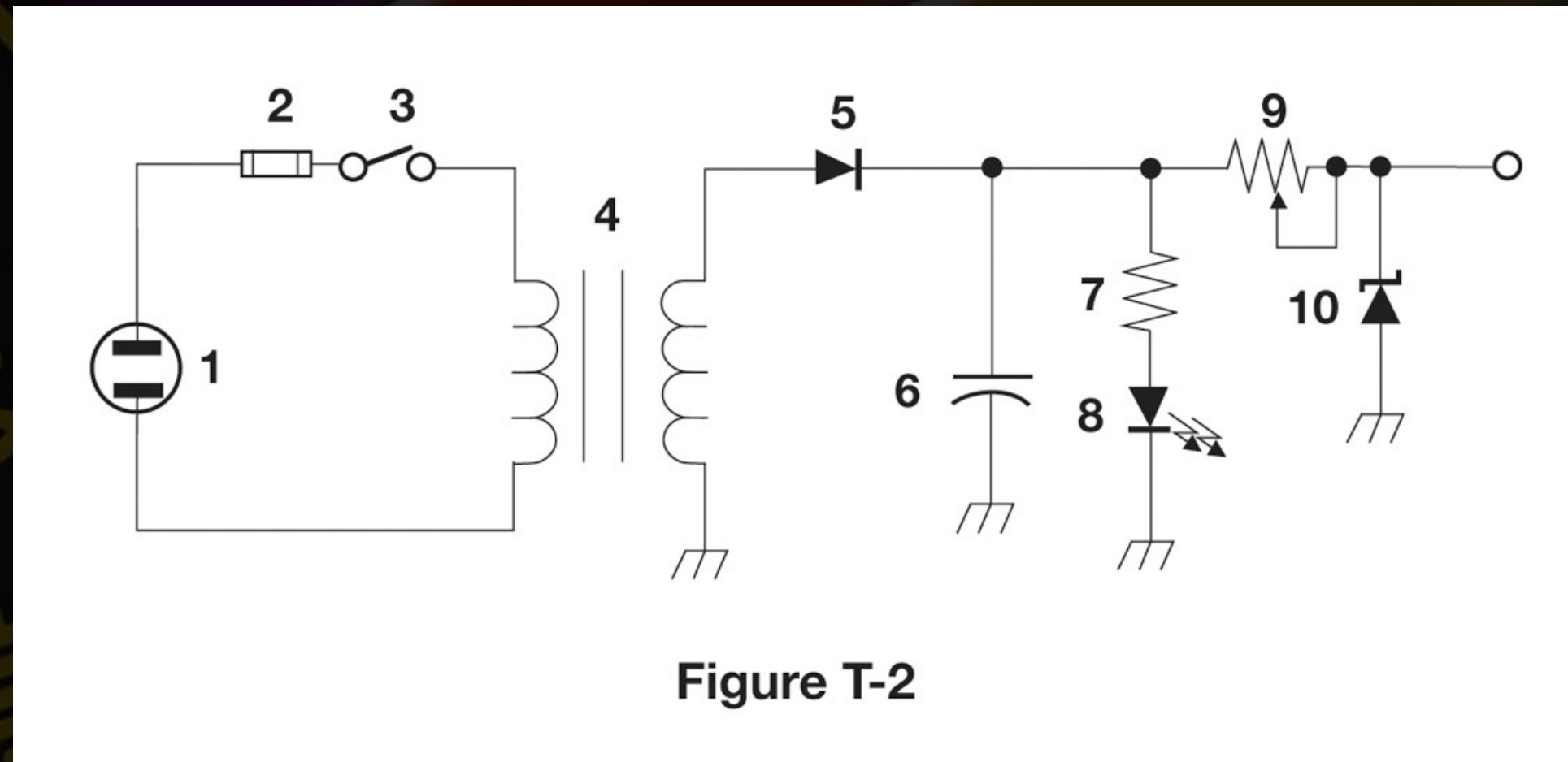


Figure T-2

Variable resistor

What is component 4 in figure T2?

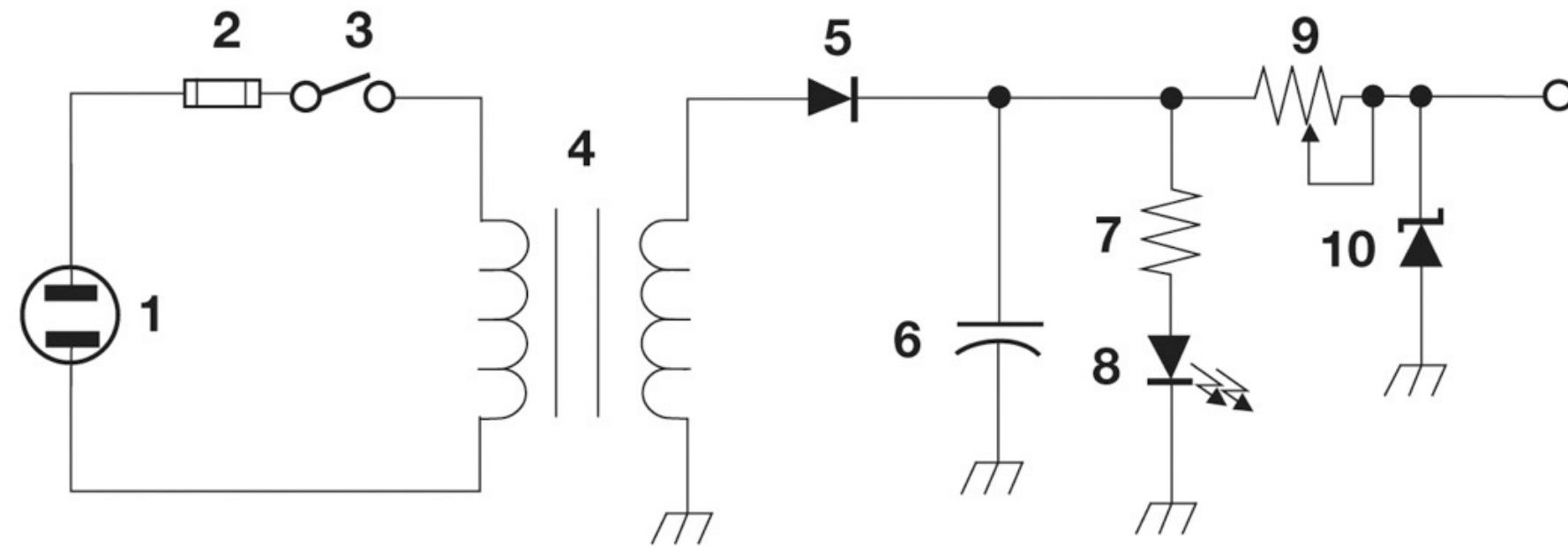


Figure T-2

What is component 4 in figure T2?

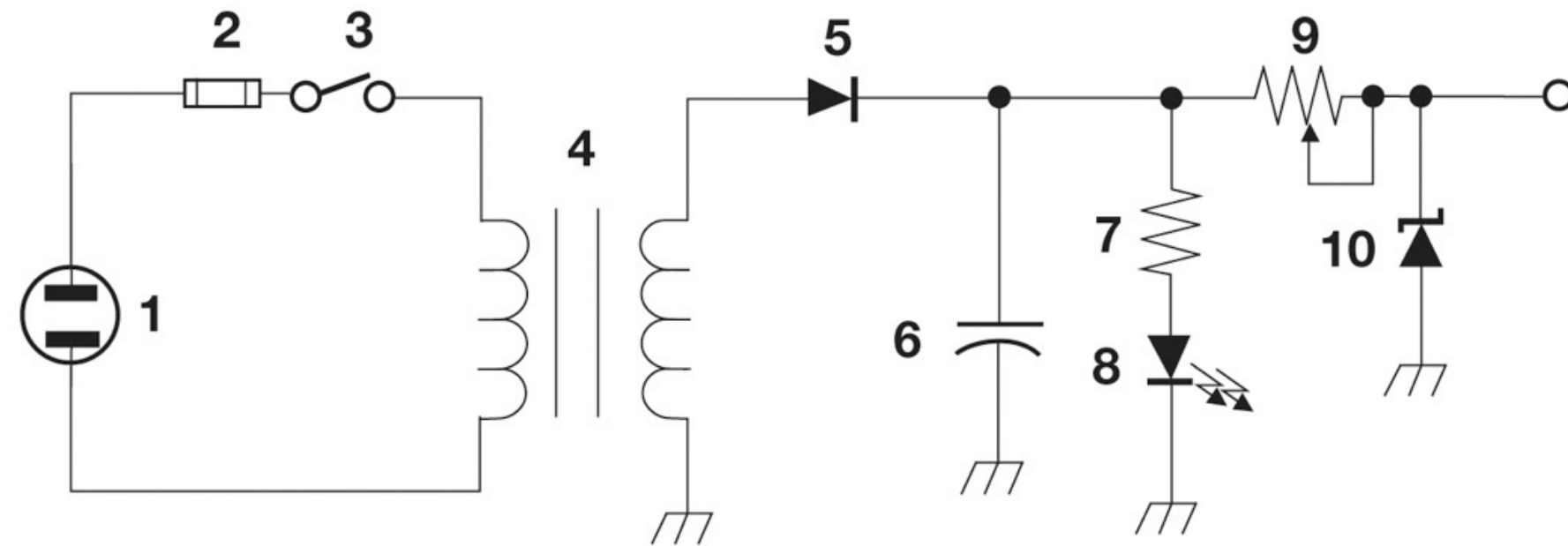


Figure T-2

Transformer

What is component 3 in figure T3?

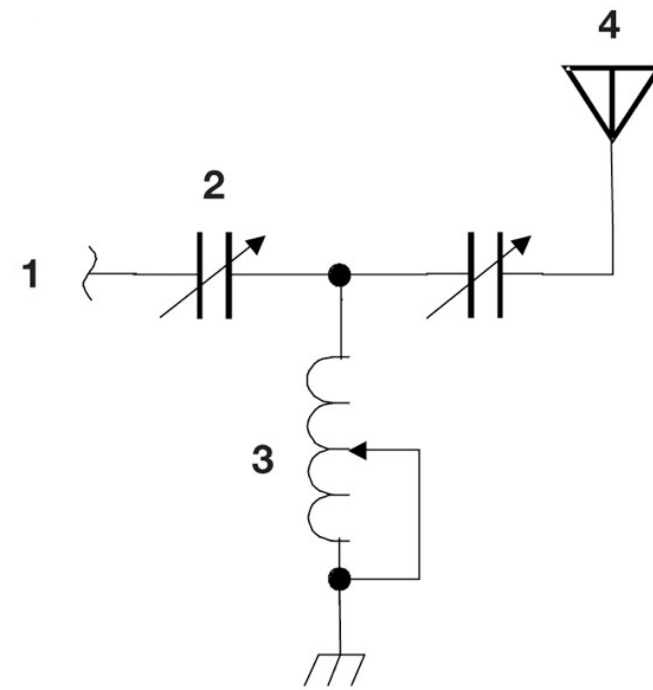


Figure T-3

What is component 3 in figure T3?

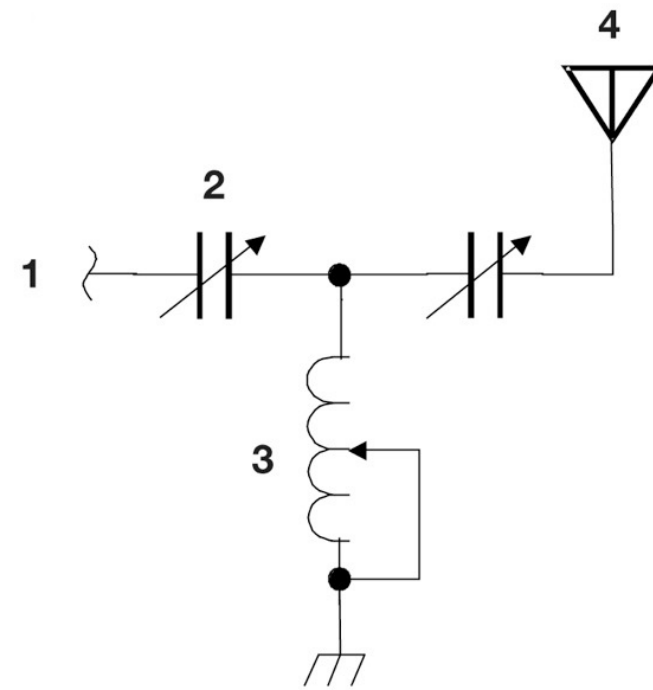


Figure T-3

Variable inductor

What is component 4 in figure T3?

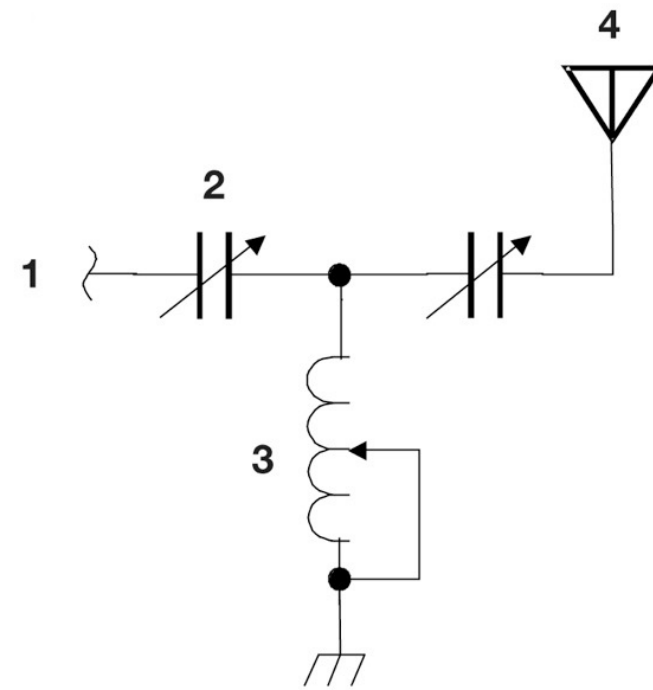


Figure T-3

What is component 4 in figure T3?

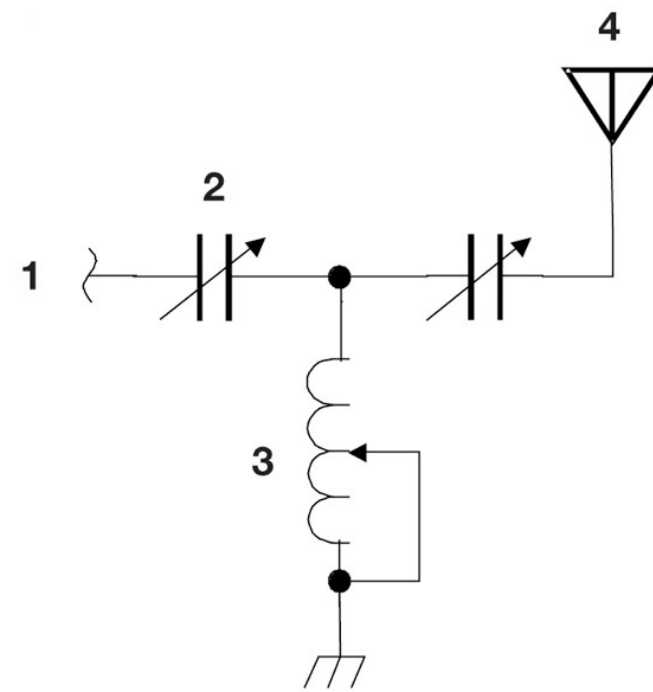


Figure T-3

Antenna

What do the symbols on an electrical circuit schematic diagram represent?

Base



What do the symbols on an electrical circuit schematic diagram represent?

Electrical components

Base




Which of the following is accurately represented in electrical circuit schematic diagrams?

Base



Which of the following is accurately represented in electrical circuit schematic diagrams?

The way components are interconnected

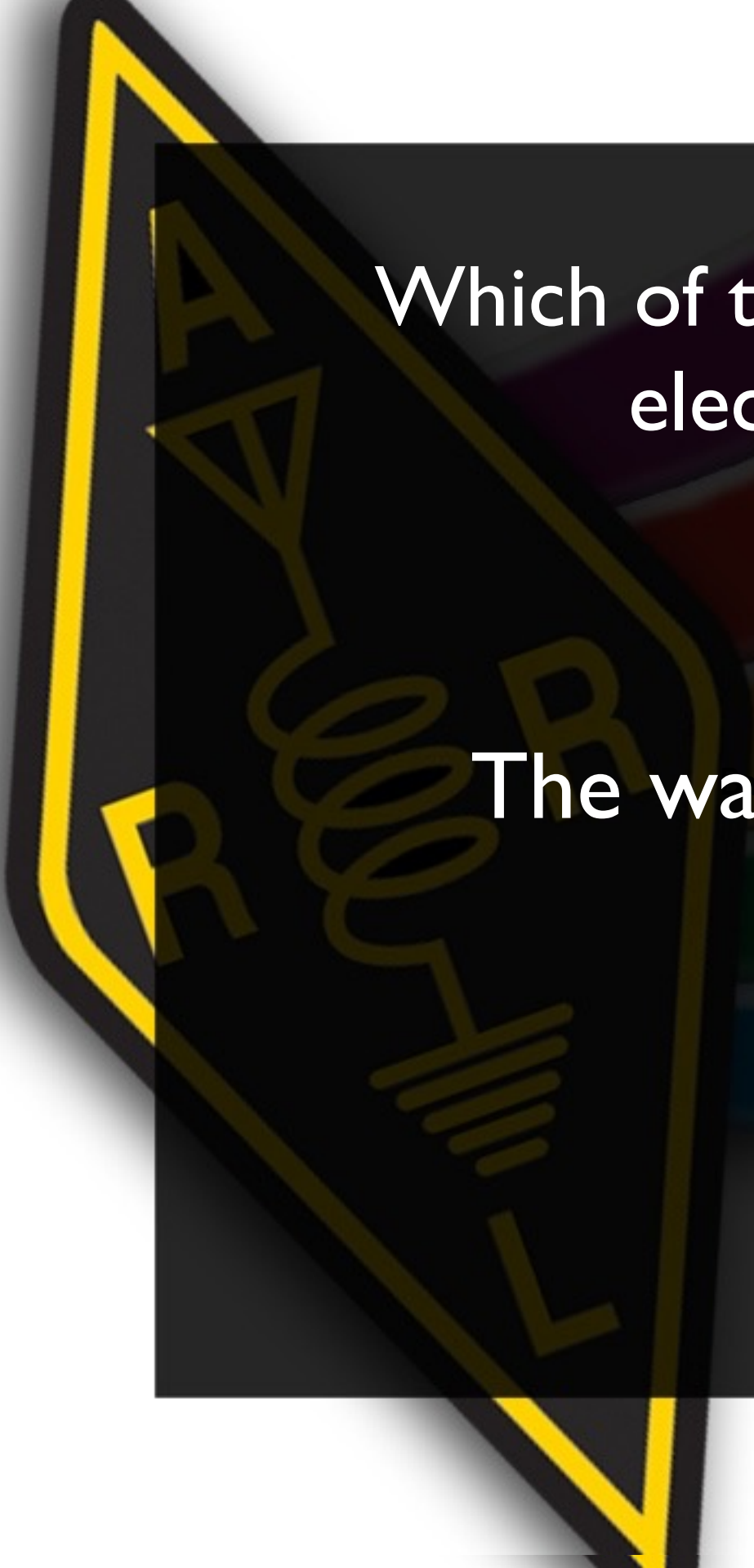

What devices or circuits change an alternating current into a varying direct current signal?

Base



What devices or circuits change an alternating current into a varying direct current signal?

Rectifier

Base



What best describes a relay?

Base





What best describes a relay?



A switch controlled by an electromagnet



What type of switch is represented by component 3 in figure T2?

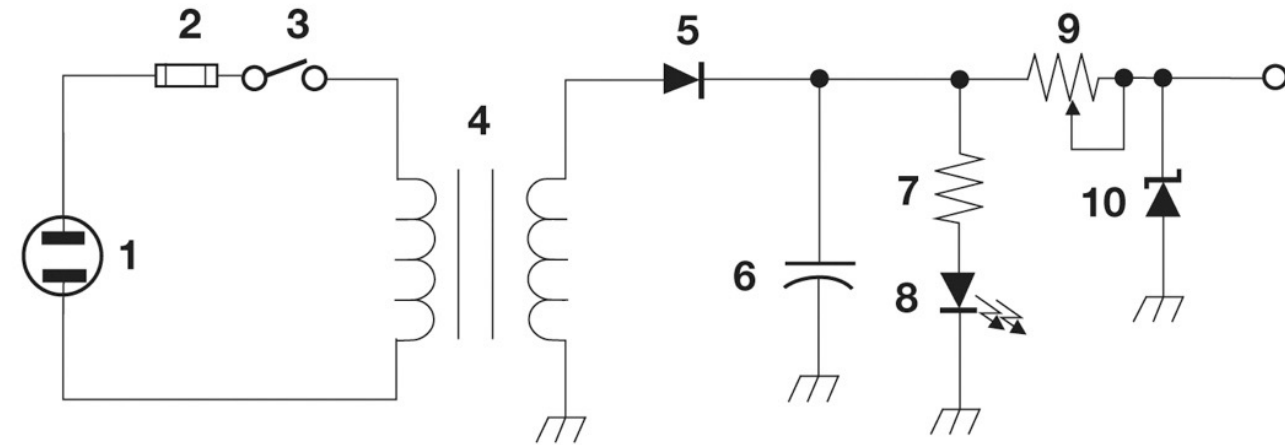


Figure T-2

What type of switch is represented by component 3 in figure T2?

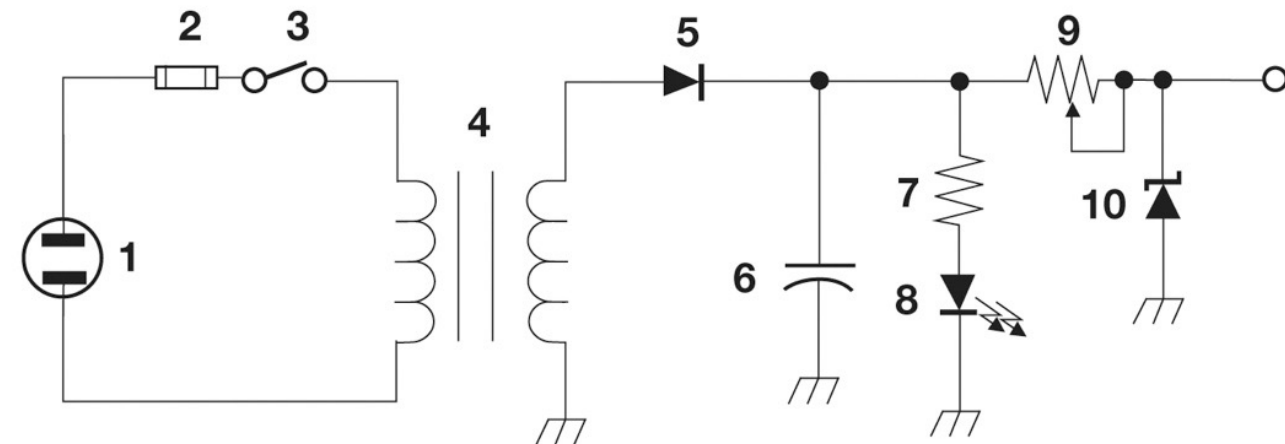


Figure T-2

Single-pole single-throw

What can be used to display signal strength on a numeric scale?

Base



What can be used to display signal strength on a numeric scale?

Meter

Base



What component is commonly used to change 120V AC house current to a lower AC voltage for other uses?


Base



What component is commonly used to change 120V AC house current to a **lower AC voltage** for other uses?

Transformer

Base

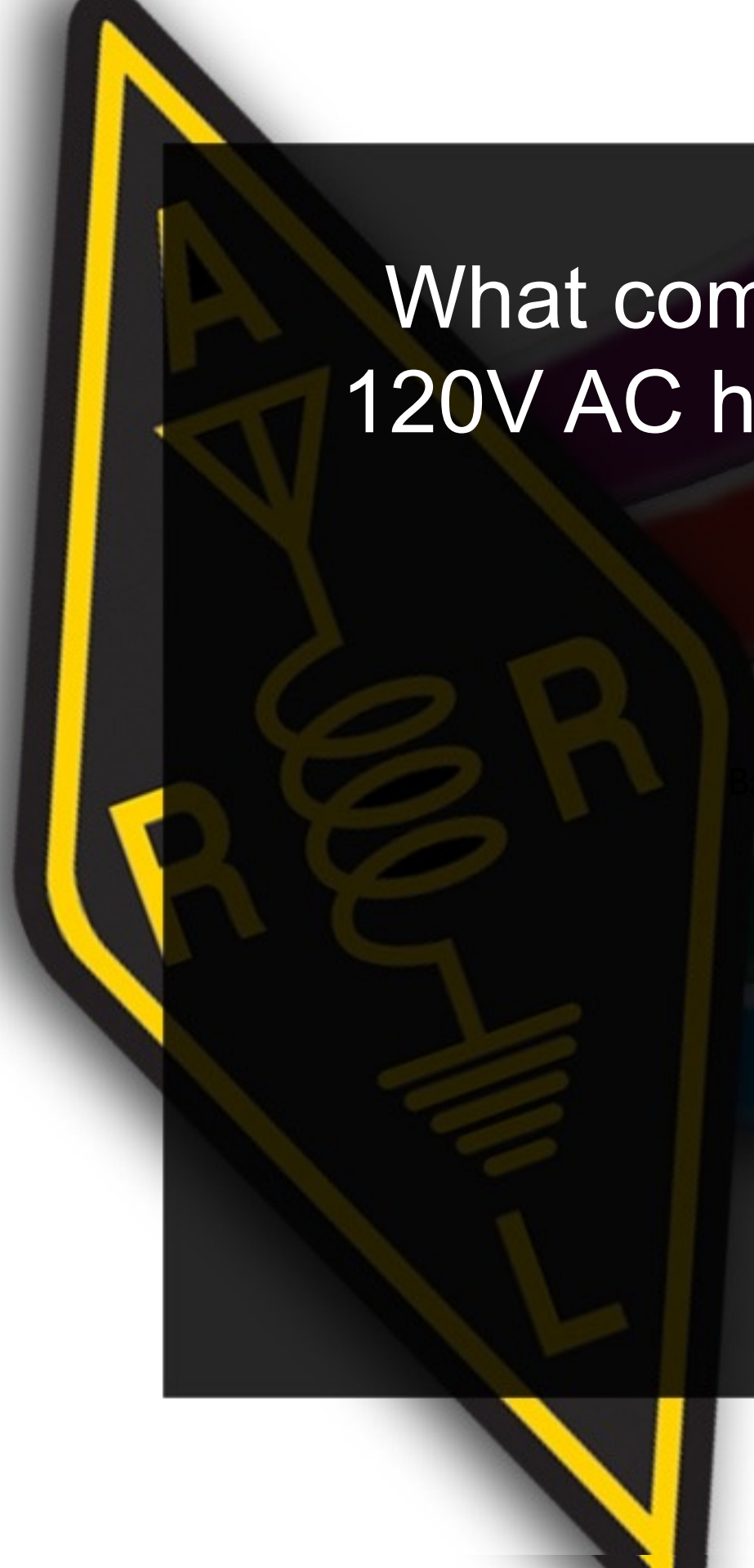

What is commonly used as a visual indicator?

Base



What is commonly used as a visual indicator?

Light Emitting Diode (LED)



What is used together with an inductor to make a tuned circuit?

Base



What is used together with an inductor to make a tuned circuit?


Capacitor

Base



What is the name of a device that combines several semiconductors and other components into one package?

Base

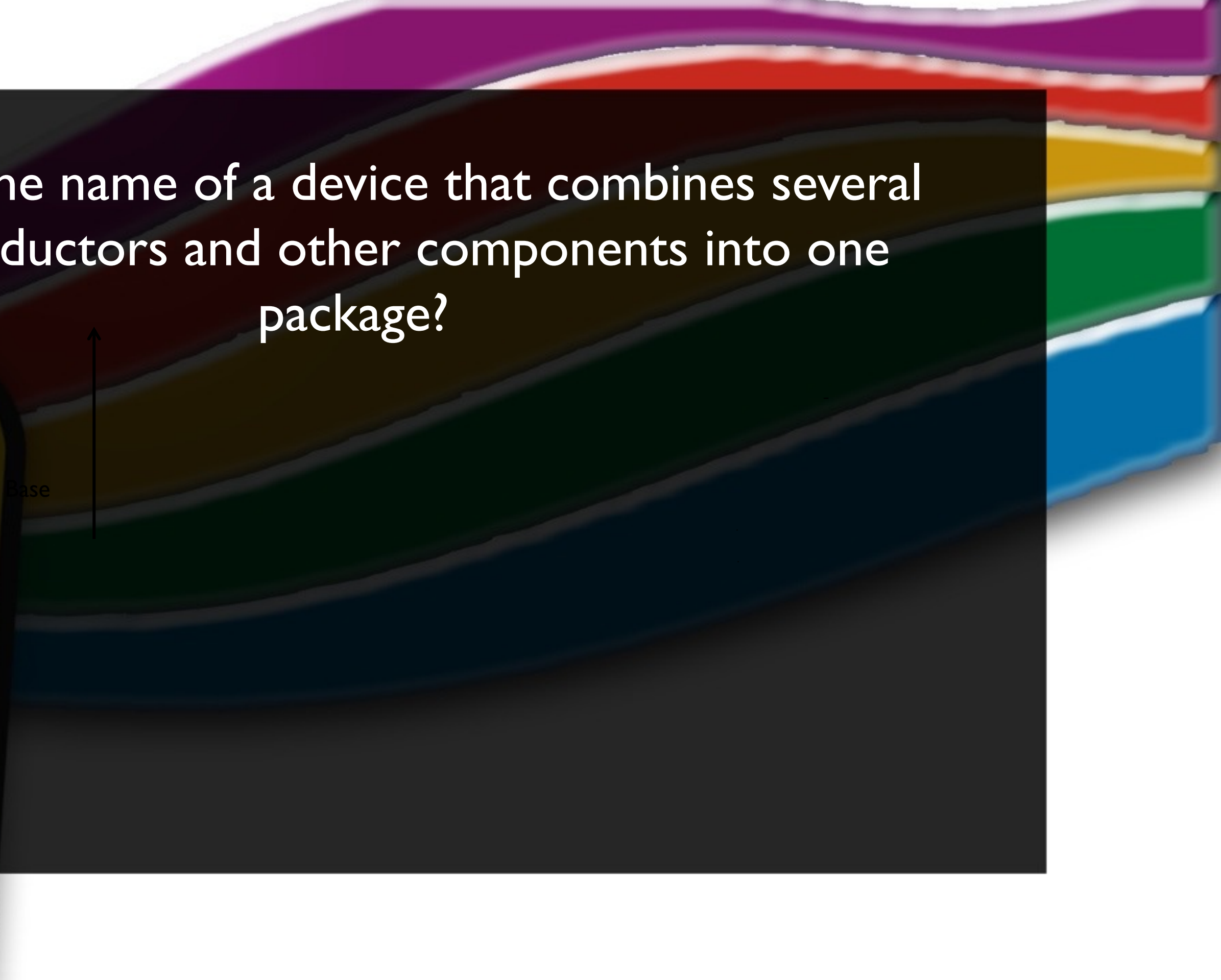

What is the name of a device that combines several semiconductors and other components into one package?

Integrated circuit

Base



What is the function of component 2 in Figure T1?

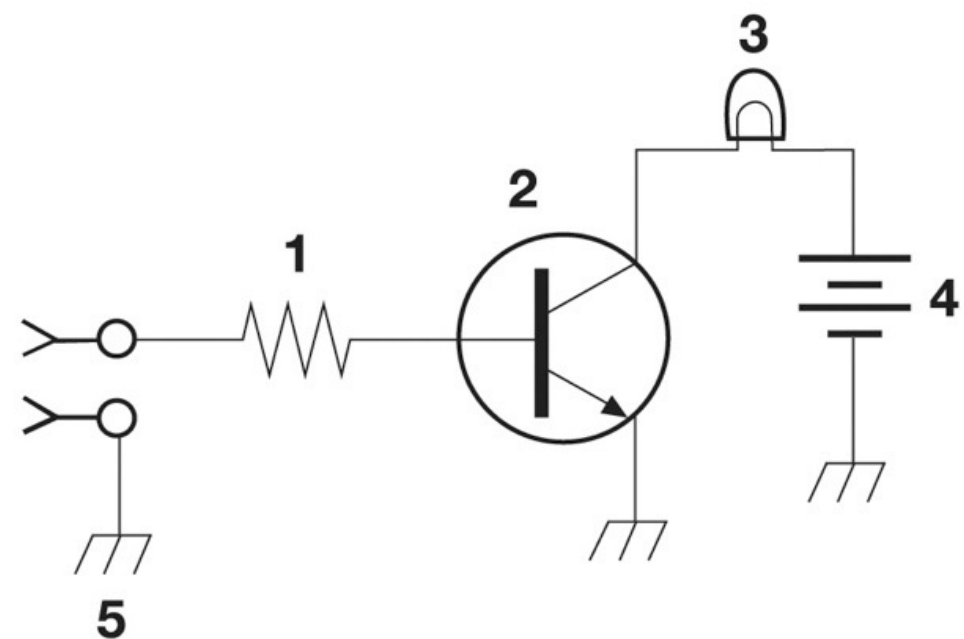


Figure T-1

What is the function of component 2 in Figure T1?

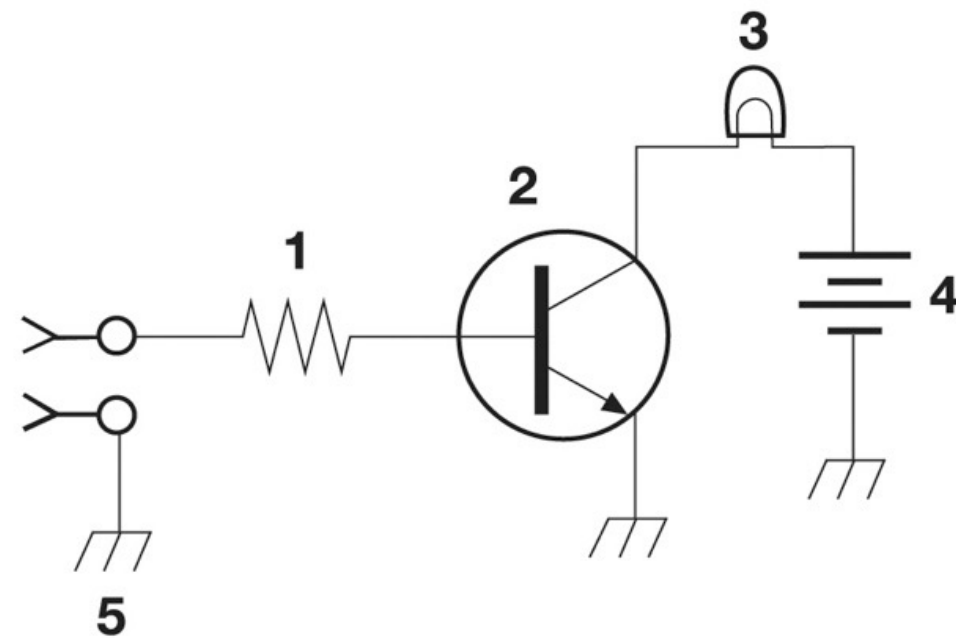


Figure T-1

Control the flow of current

What is a simple resonant or tuned circuit?



Base



What is a simple resonant or tuned circuit?

An inductor and a capacitor connected in series
or parallel to form a filter



What is the purpose of a fuse in an electrical circuit?

Base






What is the purpose of a fuse in an electrical circuit?

To interrupt power in case of overload

Why is it unwise to install a 20-ampere fuse in the place of a 5-ampere fuse?

Base



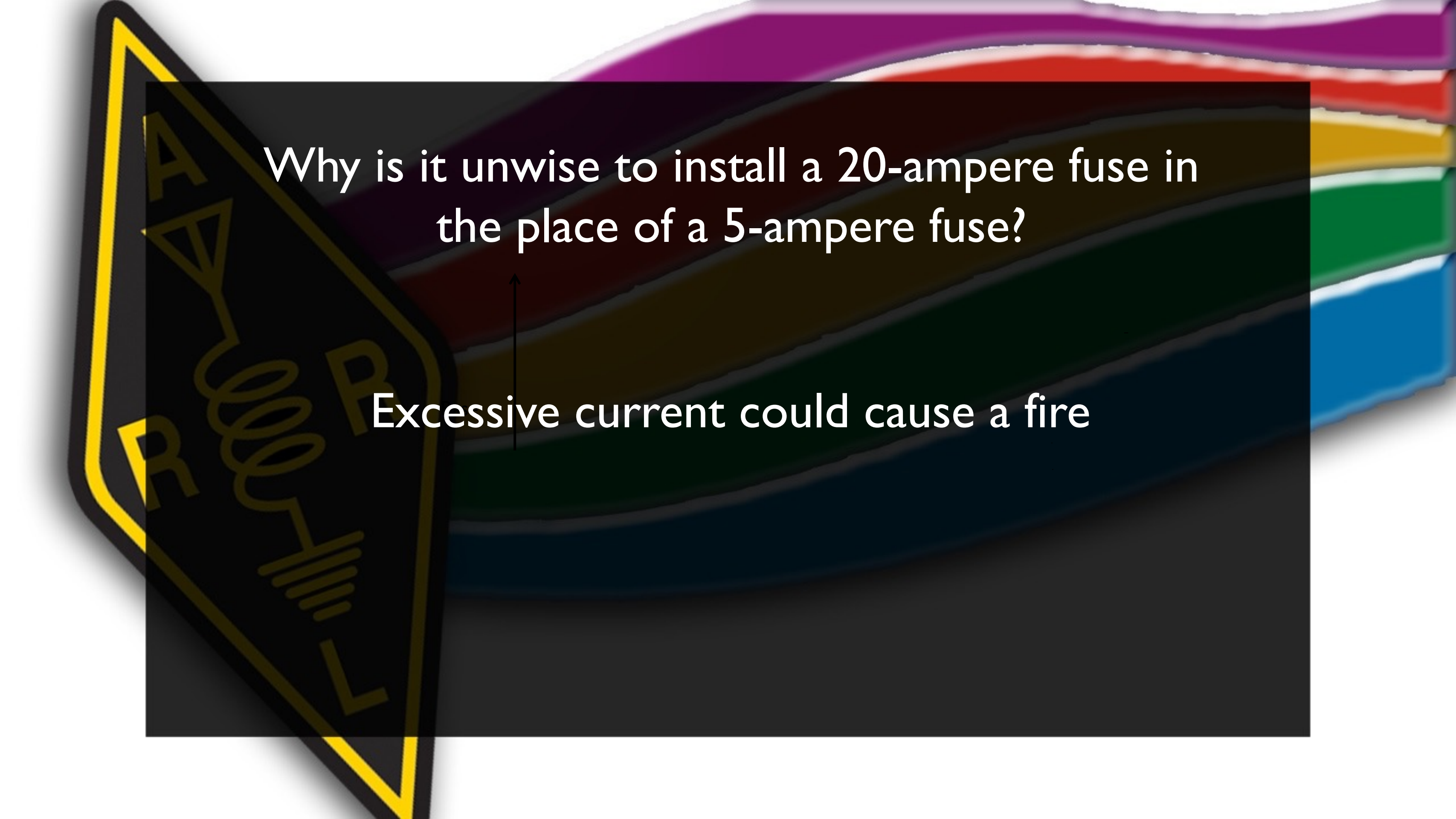

Why is it unwise to install a 20-ampere fuse in the place of a 5-ampere fuse?



Excessive current could cause a fire





End of Module 6